

Fundamental (Nonlinear) Circuit Elements: Positive Feedback And Relaxation Oscillations

Bharathwaj Muthuswamy

Assistant Professor of Electrical Engineering

Milwaukee School of Engineering

BS (2002); MS (2005); PhD (2009) in EECS from the University of California, Berkeley


Research Interests : Nonlinear Dynamics, Embedded Systems and Education

muthuswamy@msoe.edu

Date : April 15th 2014


Goal(s) of Lecture

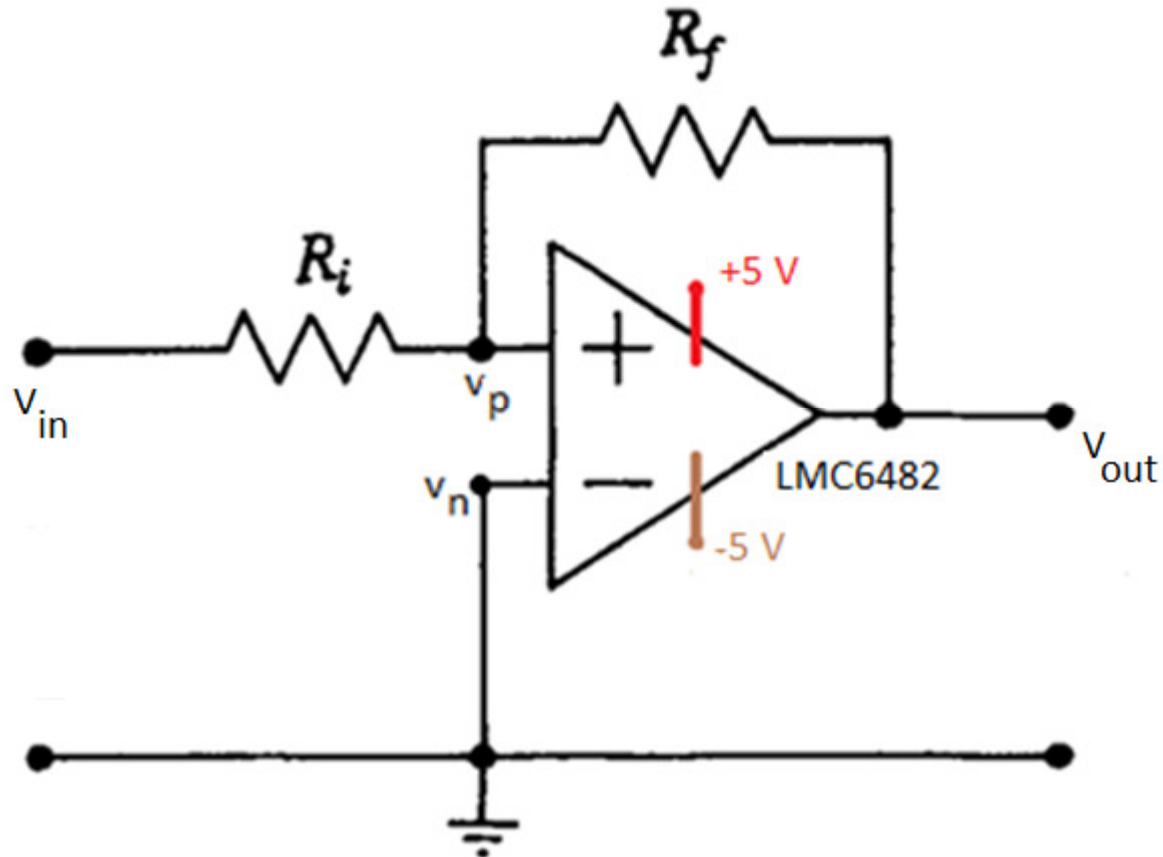Sketch V_{out} vs V_{in} for the circuit below. Verify your analysis experimentally. Explain any discrepancies between your analysis and experimental results.




Goal(s) of Lecture


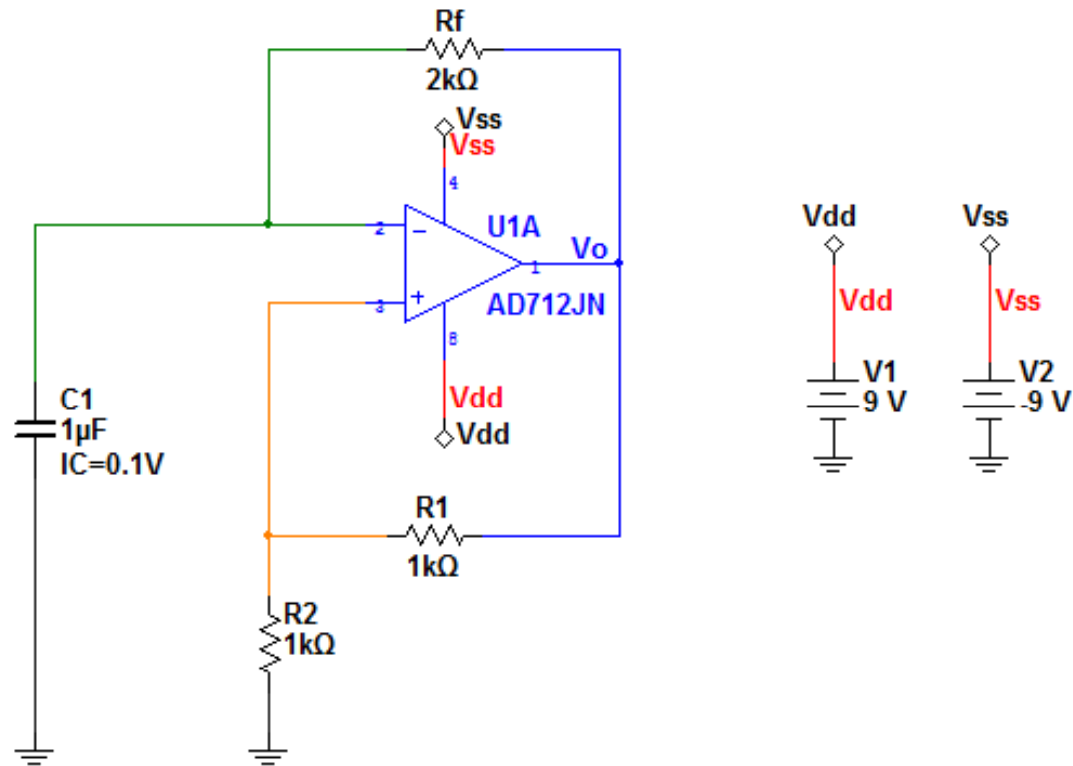
Analytically determine the period and duty cycle in the circuit below.



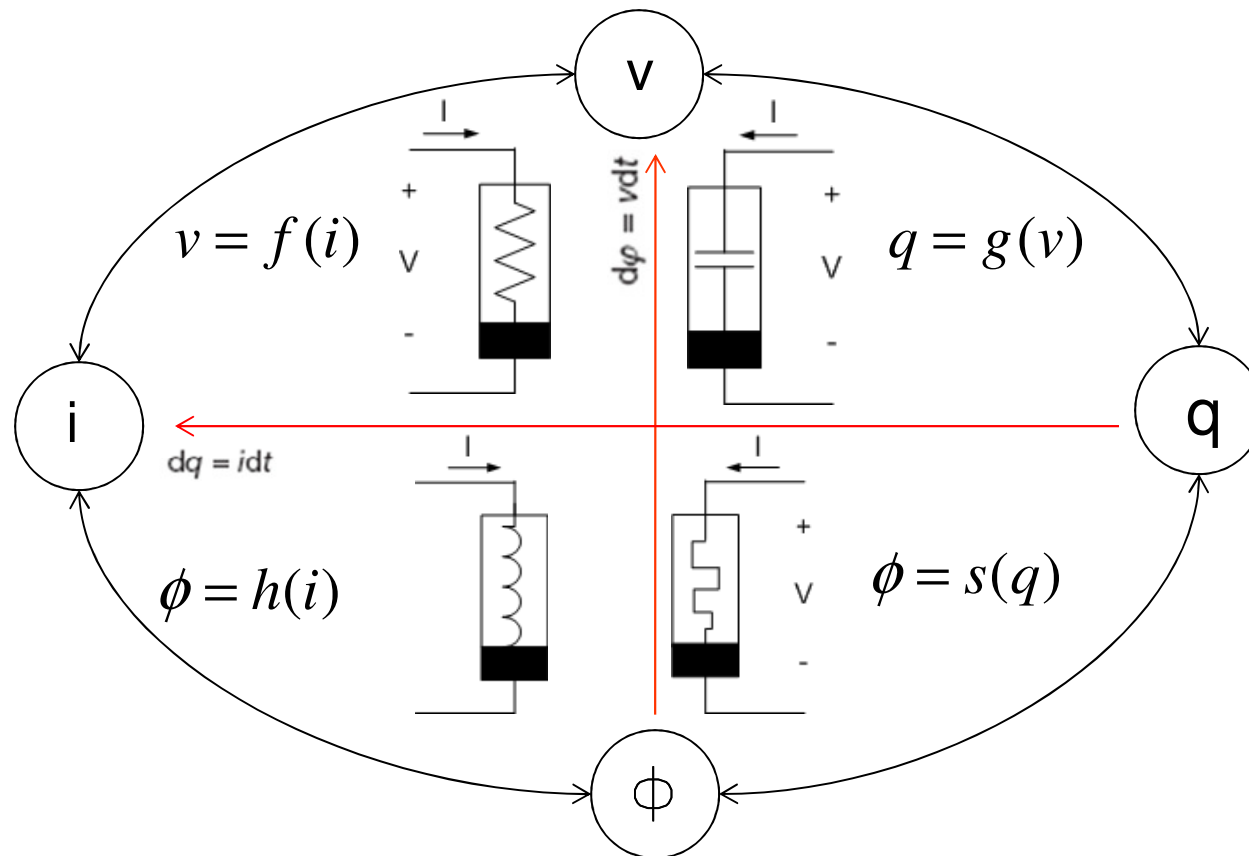“Review” : The Fundamental Circuit Elements




“Review” : The Operational Amplifier

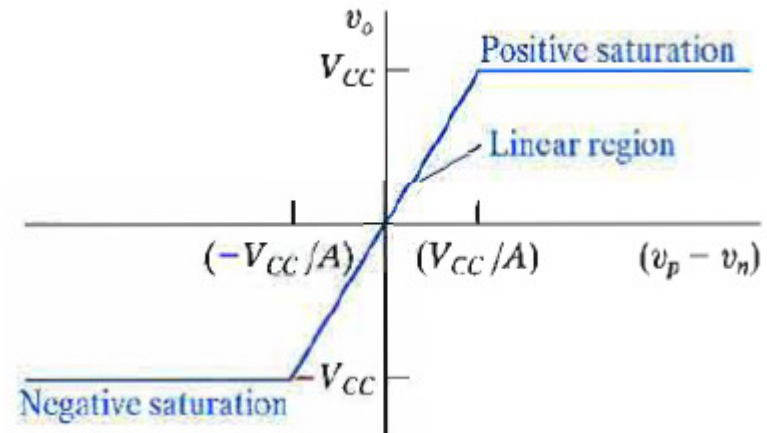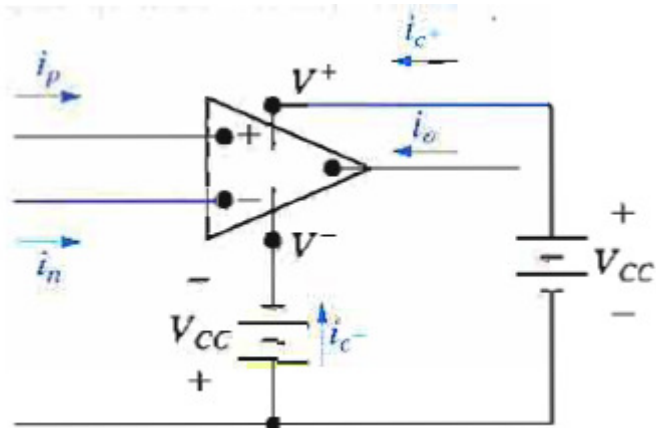

$$v_o = \begin{cases} -V_{CC} & A(v_p - v_n) < -V_{CC}, \\ A(v_p - v_n) & -V_{CC} \leq A(v_p - v_n) \leq +V_{CC}, \\ +V_{CC} & A(v_p - v_n) > +V_{CC}. \end{cases}$$

Step 1: Understand Problem

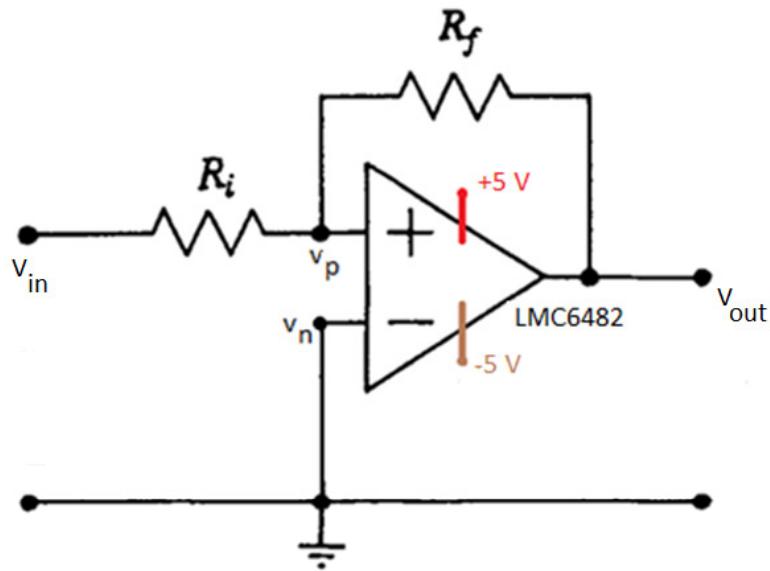


**This circuit (system) is
non-dynamical!**

Equilibrium Points are:



Reference :

<http://www.learner.org/courses/mathilluminated/units/13/textbook/03.php>

Stable equilibrium

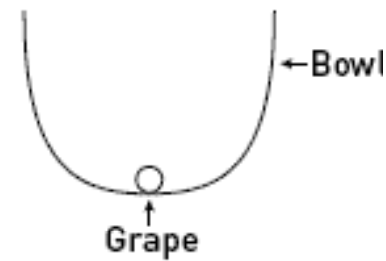

Unstable equilibrium

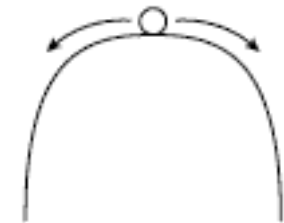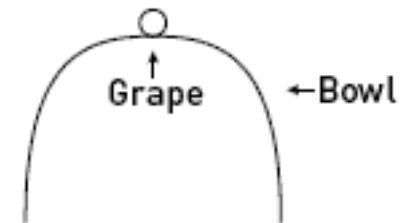

Step 2: Devise a Plan

1. Derive V_{out} vs V_{in} using op-amp golden rules
2. Interpret the results
3. Devise an experiment to confirm our derivation (theory)

Step 3 (a): Carry out the plan – Derive V_{out} vs V_{in} (linear region)

Assuming op-amp is in the linear region: $v_p = v_n$


Applying KCL and Ohm's law at v_p :

$$\frac{v_{in} - v_p}{R_i} = \frac{v_p - v_{out}}{R_f}$$

$$\Rightarrow \frac{v_{in} - v_n}{R_i} = \frac{v_p - v_{out}}{R_f}$$

$$\Rightarrow \frac{v_{in}}{R_i} = \frac{-v_{out}}{R_f}$$

Hence $v_{out} = -2v_{in}$

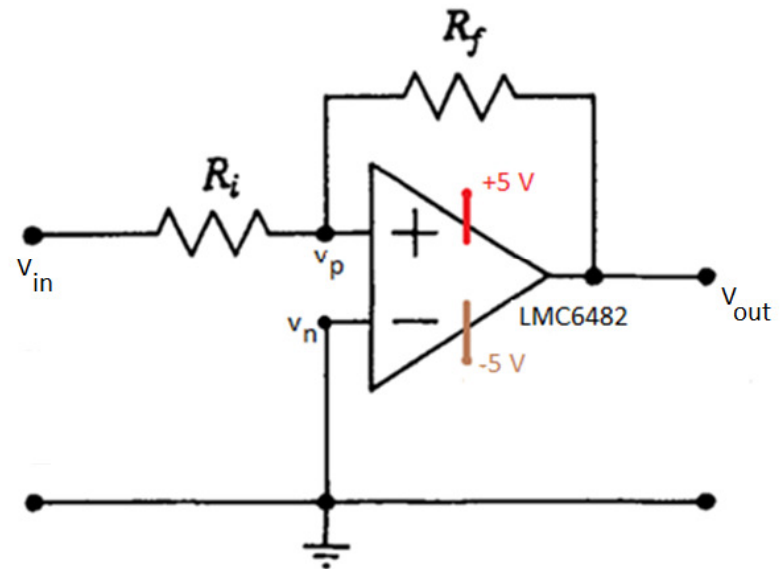


Step 3 (b): Carry out the plan – Derive V_{out} vs V_{in} (positive saturation region)

Since op-amp is assumed to be in positive saturation: $v_{out} = +v_{CC}$, $v_p \geq v_n$

Applying KCL and Ohm's law at v_p :

$$\frac{v_{in} - v_p}{R_i} = \frac{v_p - v_{out}}{R_f}$$
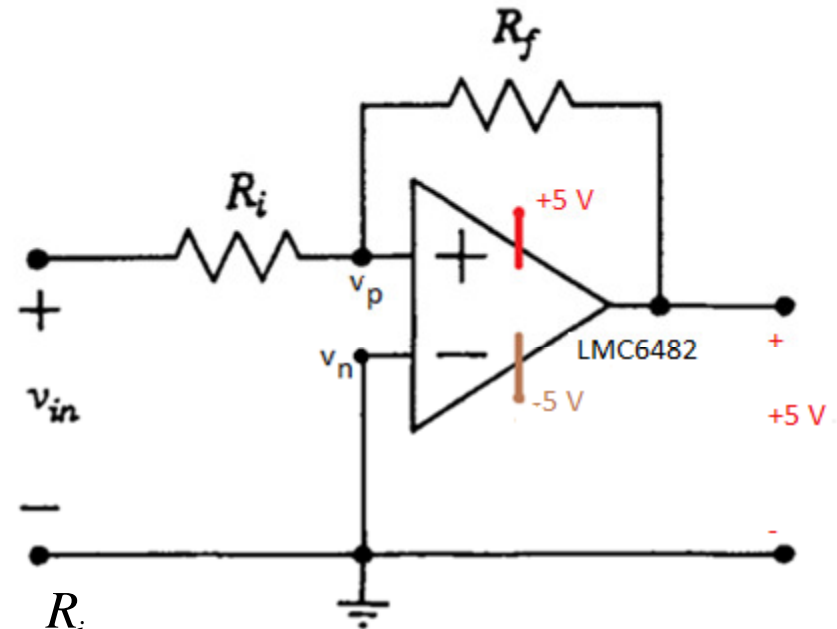
$$\Rightarrow v_p = \frac{v_{in} + \frac{R_i}{R_f} v_{CC}}{1 + \frac{R_i}{R_f}}$$



Now, $v_{out} = +v_{CC}$ if $v_p \geq v_n \Rightarrow v_{out} = +v_{CC}$ if $\frac{v_{in} + \frac{R_i}{R_f} v_{CC}}{1 + \frac{R_i}{R_f}} \geq 0$

Hence: $v_{out} = 5$ if $v_{in} \geq -2.5$ V


Step 3 (c): Carry out the plan – Derive V_{out} vs V_{in} (negative saturation region)

Since op-amp is assumed to be in negative saturation ($v_{CC} > 0$): $v_{out} = -v_{CC}$, $v_p \leq v_n$

Applying KCL and Ohm's law at v_p :

$$\frac{v_{in} - v_p}{R_i} = \frac{v_p - v_{out}}{R_f}$$
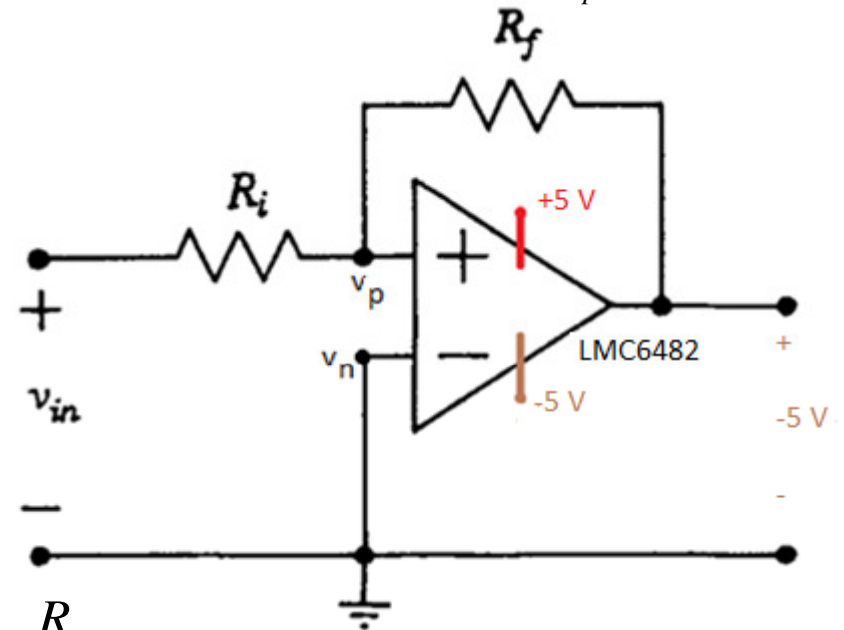
$$\Rightarrow v_p = \frac{v_{in} - \frac{R_i}{R_f} v_{CC}}{1 + \frac{R_i}{R_f}}$$




Now, $v_{out} = -v_{CC}$ if $v_p \leq v_n \Rightarrow v_{out} = -v_{CC}$ if $\frac{v_{in} - \frac{R_i}{R_f} v_{CC}}{1 + \frac{R_i}{R_f}} \leq 0$


Hence: $v_{out} = -5$ if $v_{in} \leq 2.5$ V

Step 3 (d): Sketch V_{out} vs V_{in}
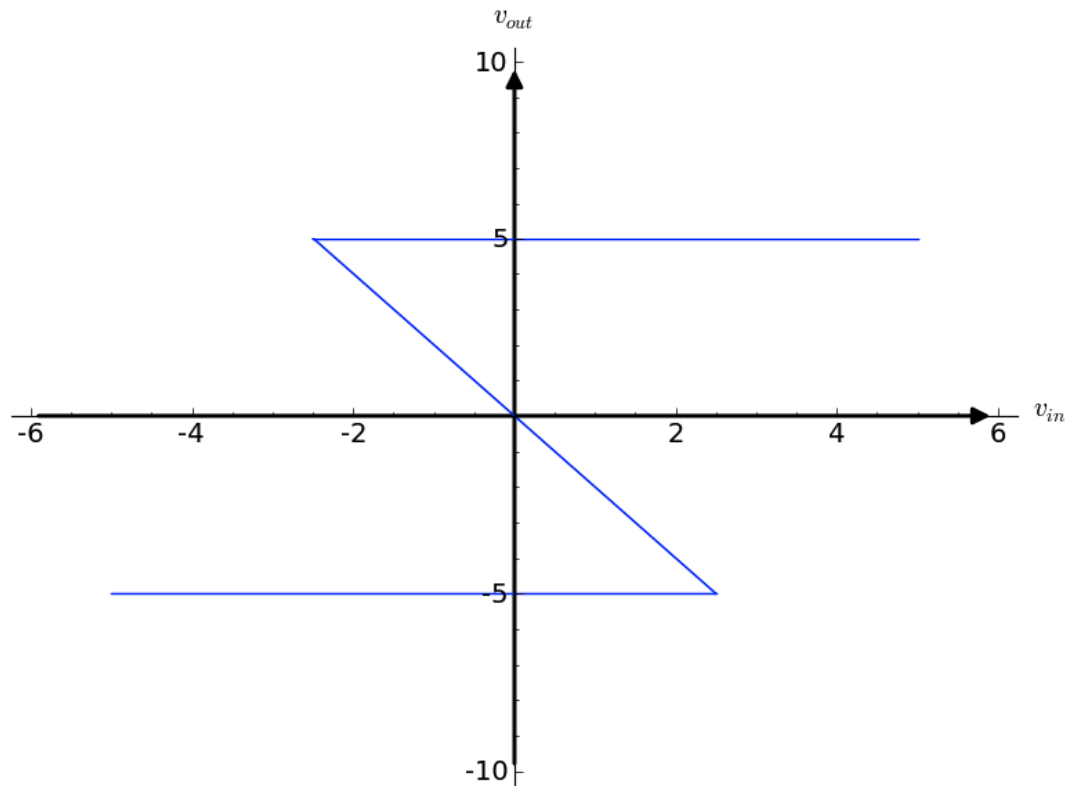
$$v_{out} = \begin{cases} 5 \text{ V} & \text{if } v_{in} \geq -2.5 \text{ V} \\ -2v_{in} & \text{if } -2.5 < v_{in} < 2.5 \\ -5 \text{ V} & \text{if } v_{in} \leq 2.5 \text{ V} \end{cases}$$







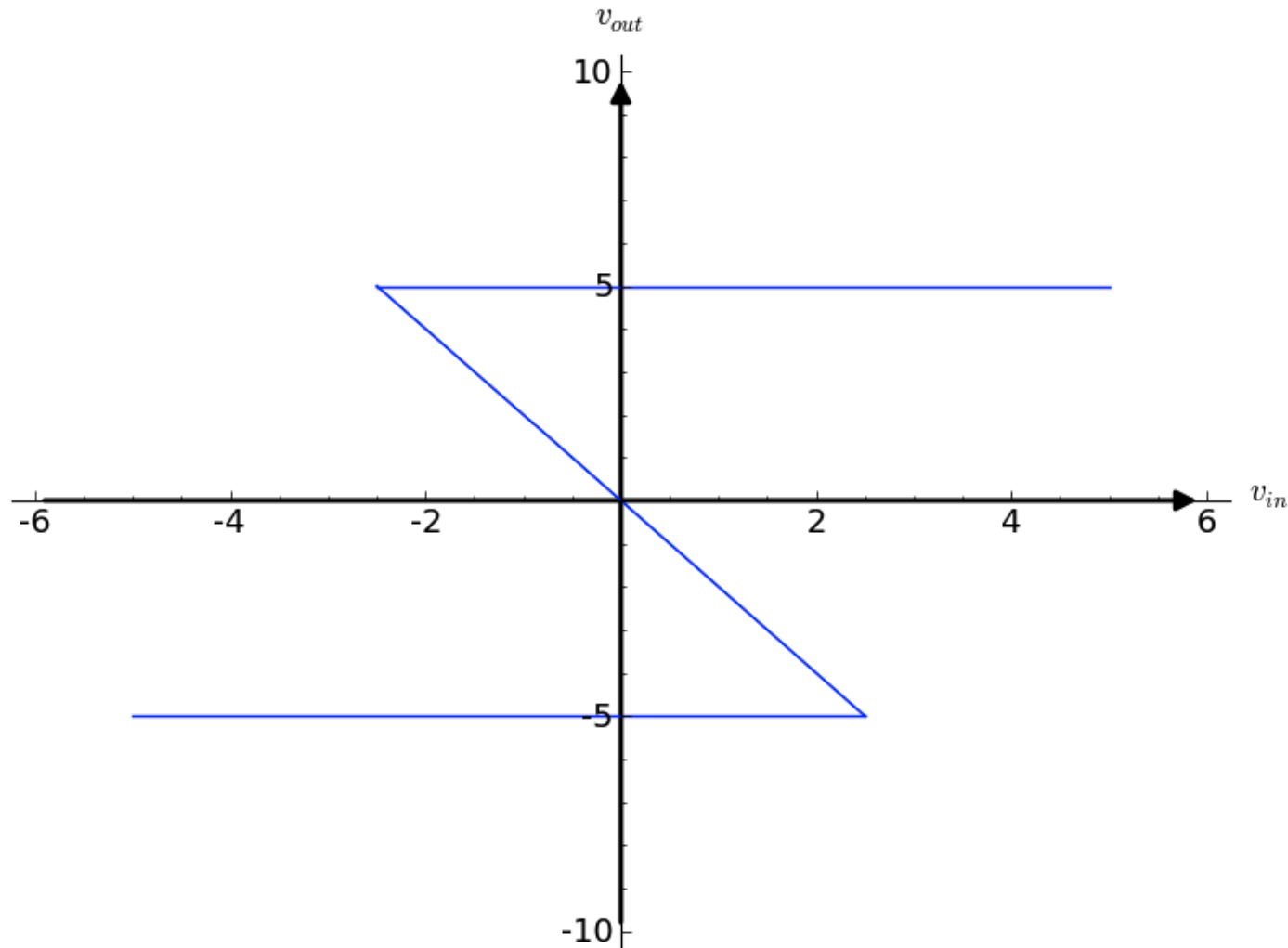Step 3 : Carry out the plan – Interpret the results







Step 4 : Check your answer


Test Circuit $u + v_{out} + v_{in} = 0$

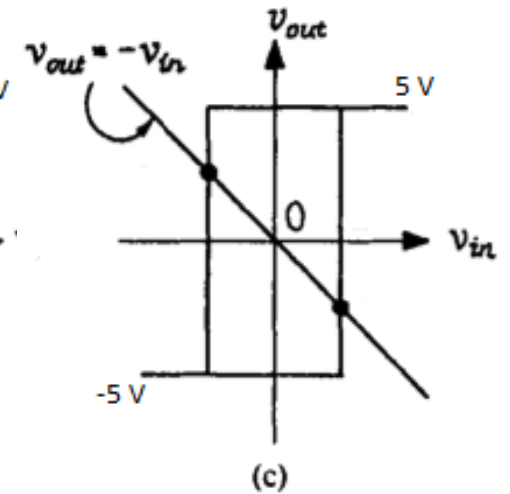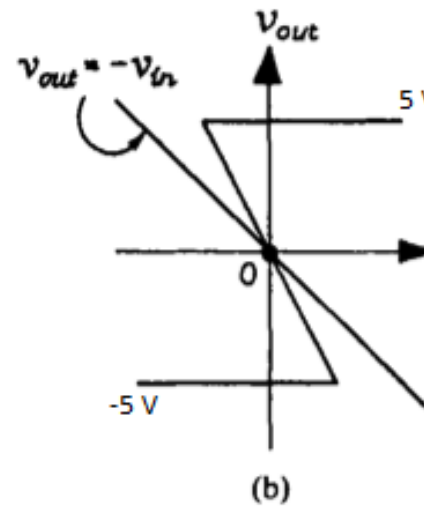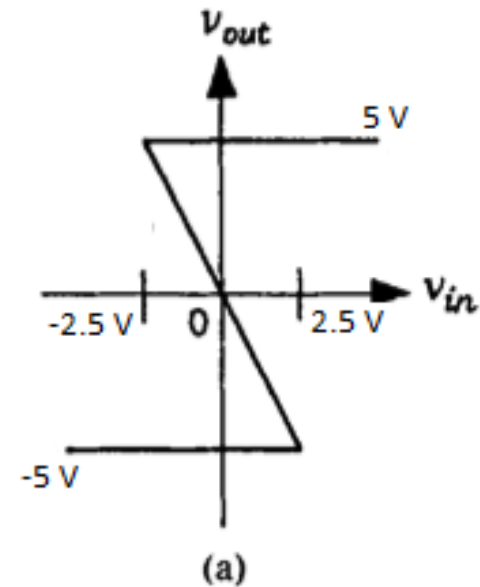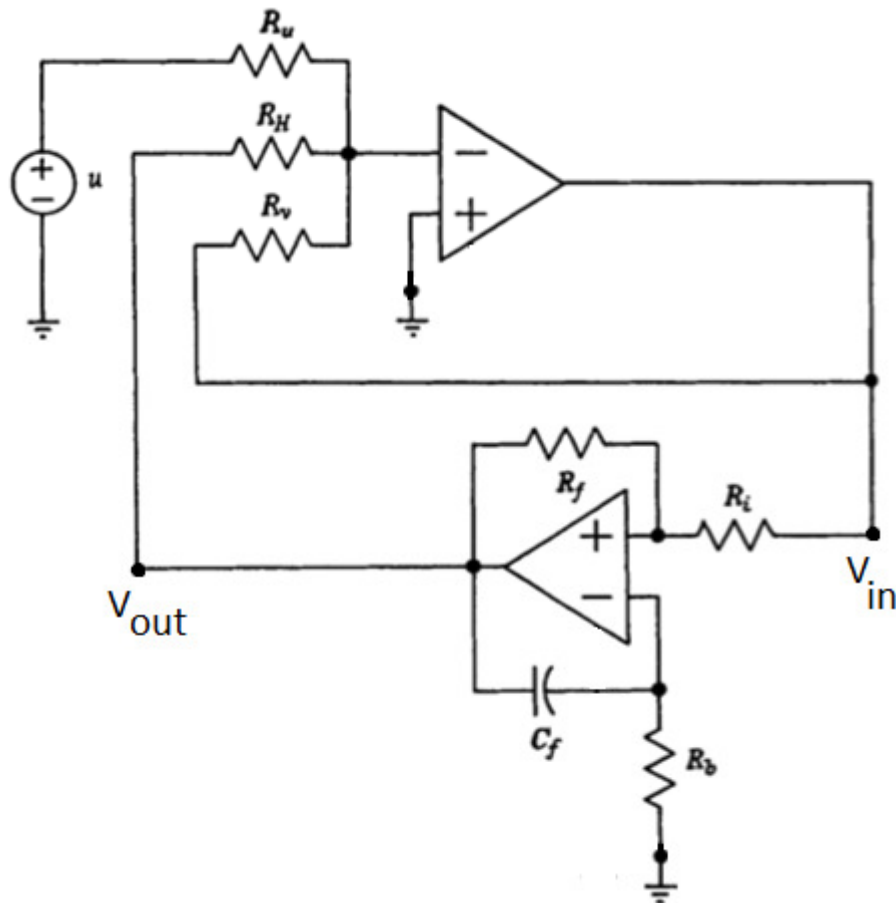


Step 4 : Check your answer (contd.)

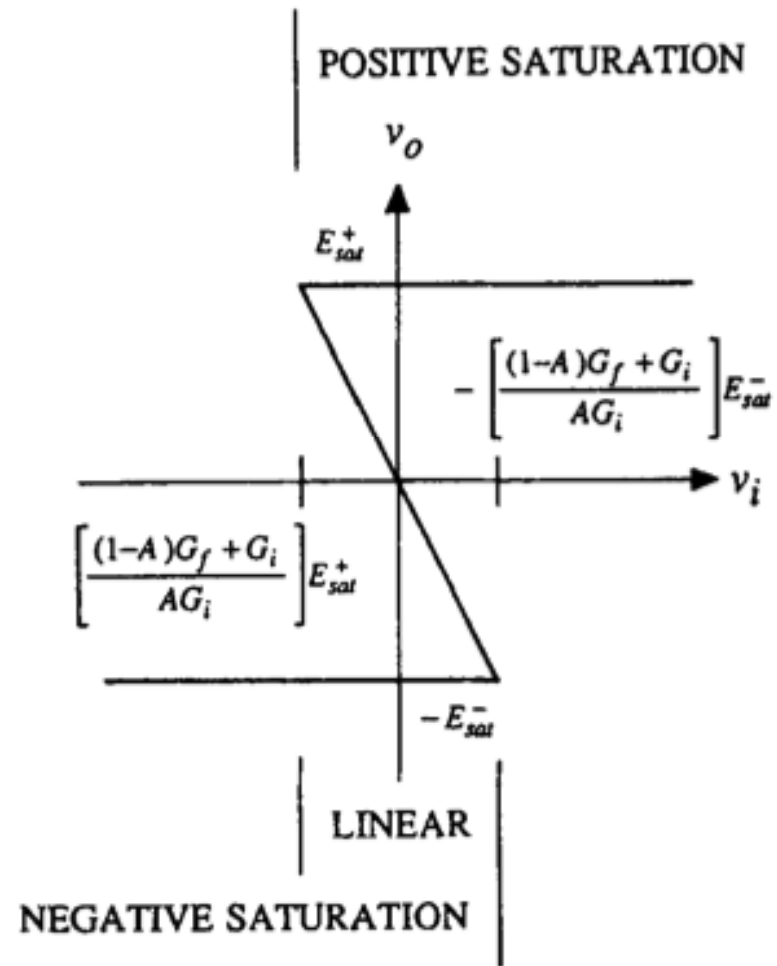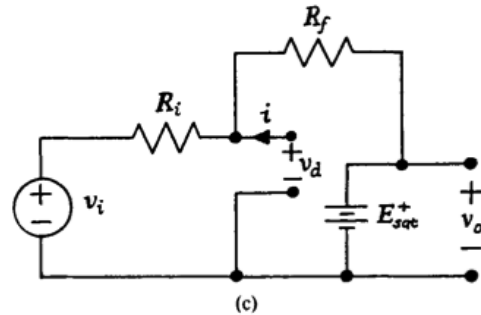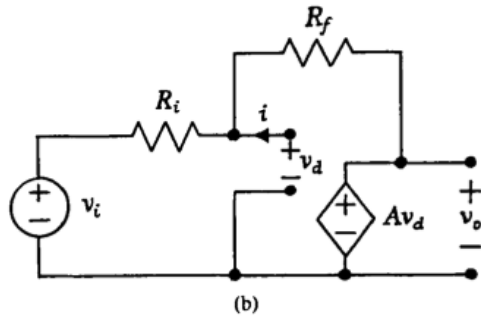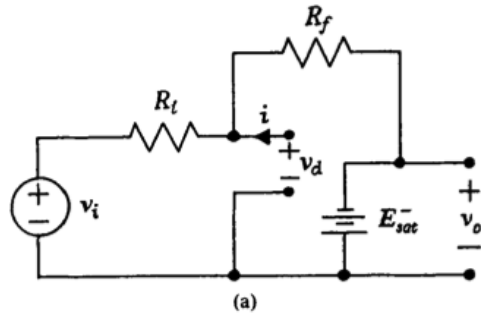

Concept of Parasitic Capacitance

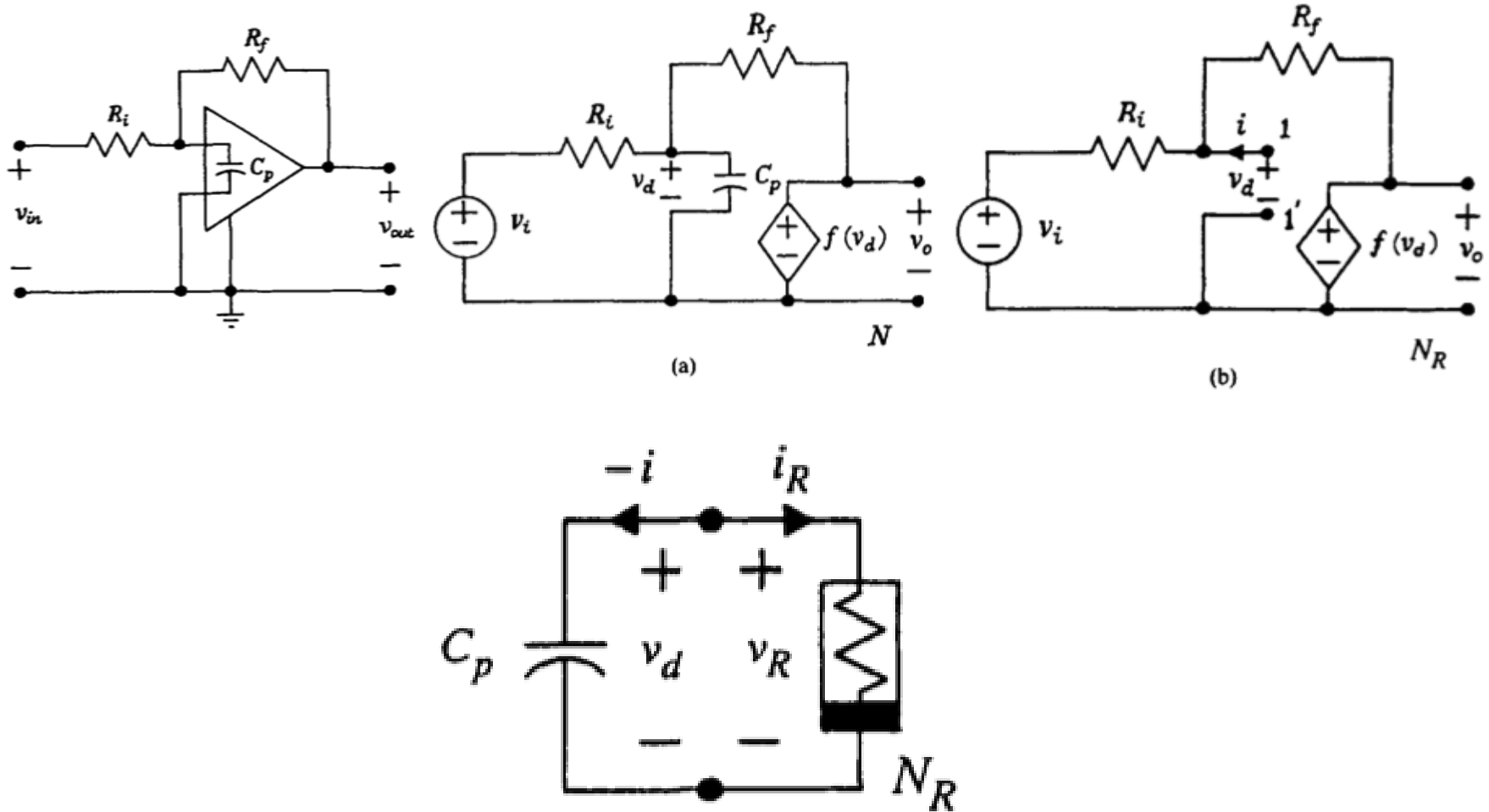


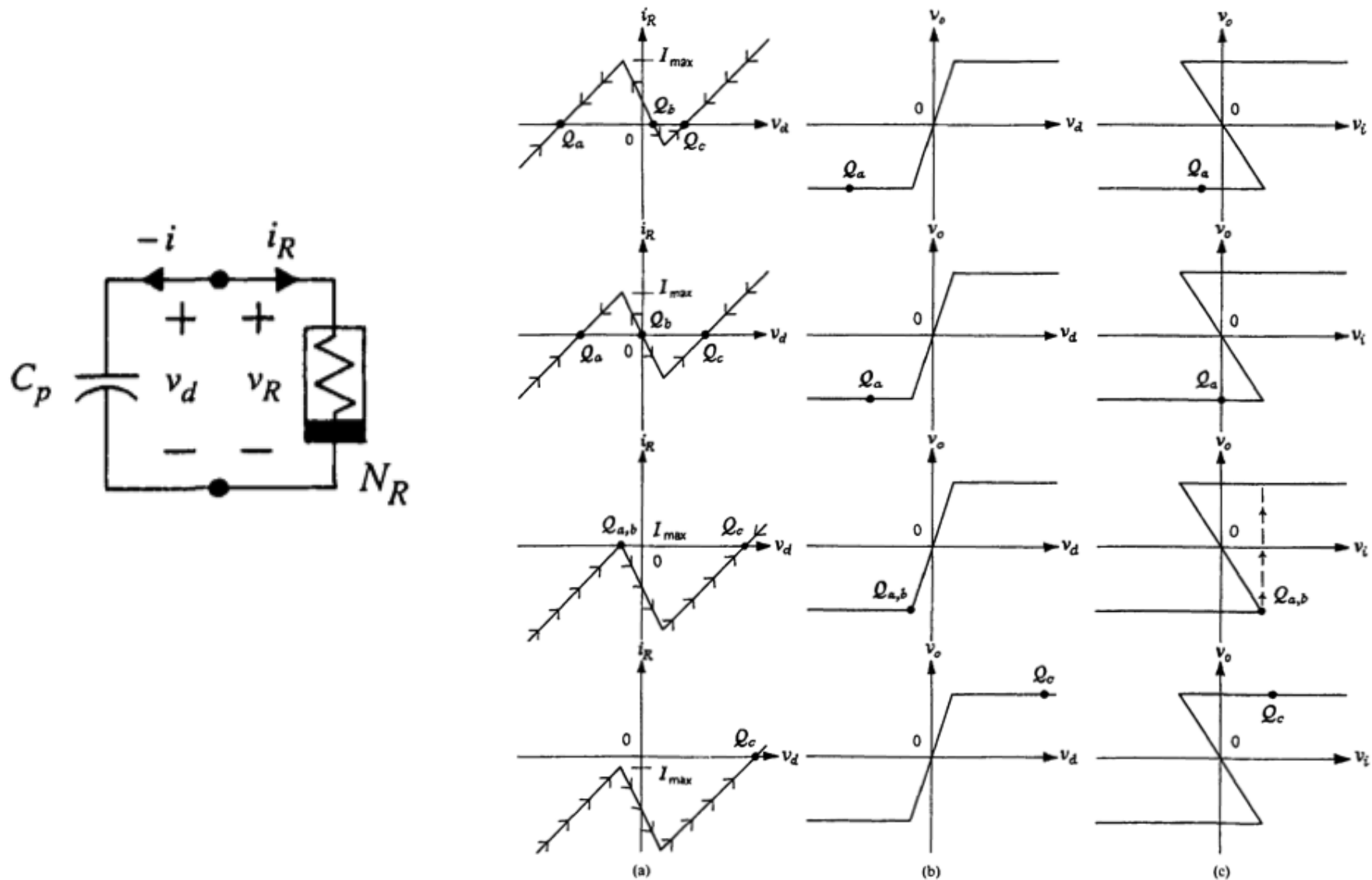Concept of Parasitic Capacitance (contd.)




Recall

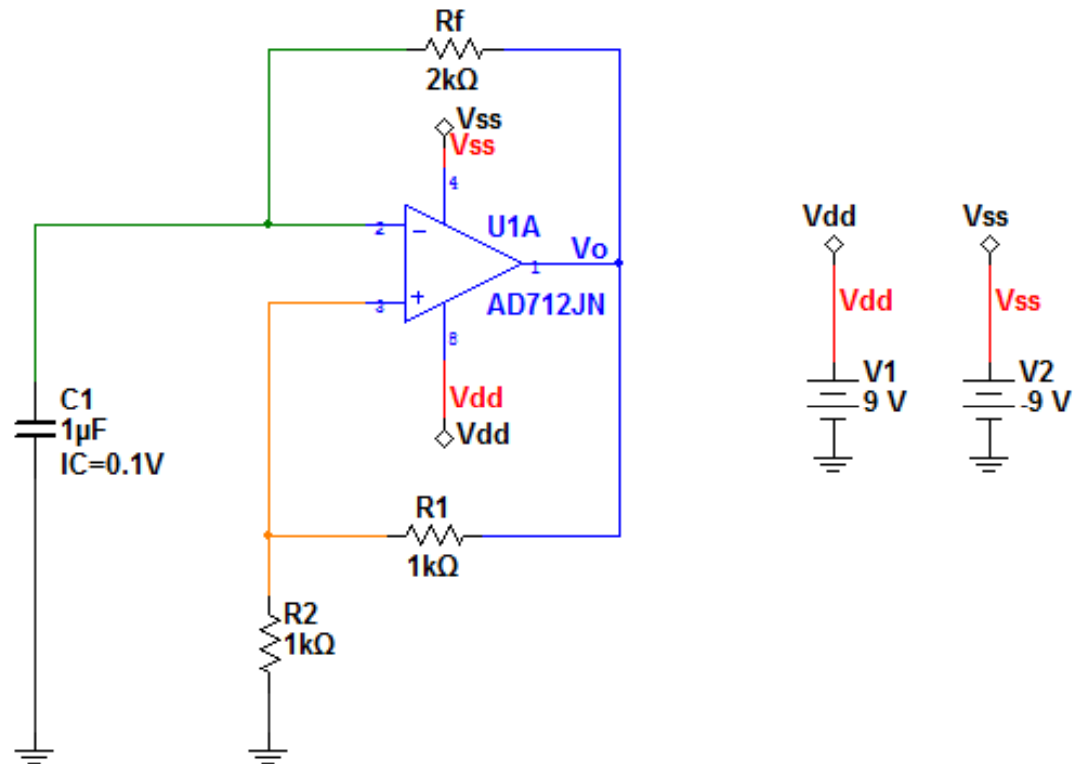
Analytically determine the period and duty cycle in the circuit below.



Definition of period and duty cycle

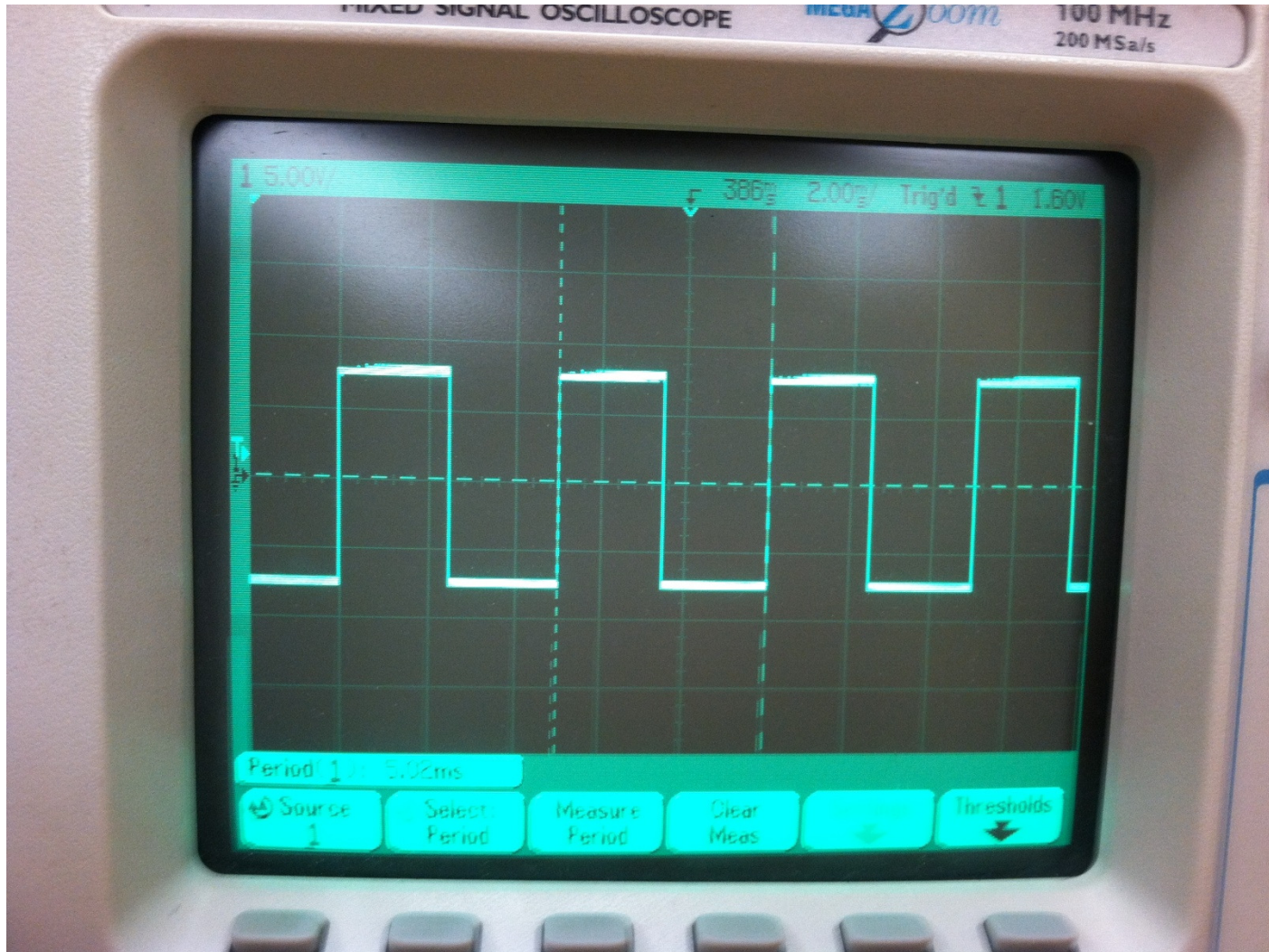

Finding the period

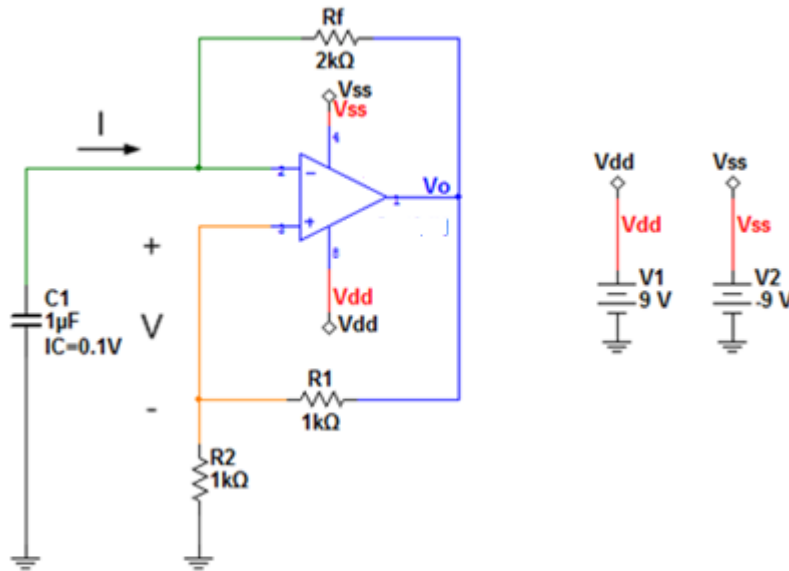


In the saturation region(s) :

$$v(t) = v_f + (v_i - v_f)e^{-t/R_f C}$$

In the positive saturation region :

$$v(t) = 9 + (-4.5 - 9)e^{-t/R_f C}$$

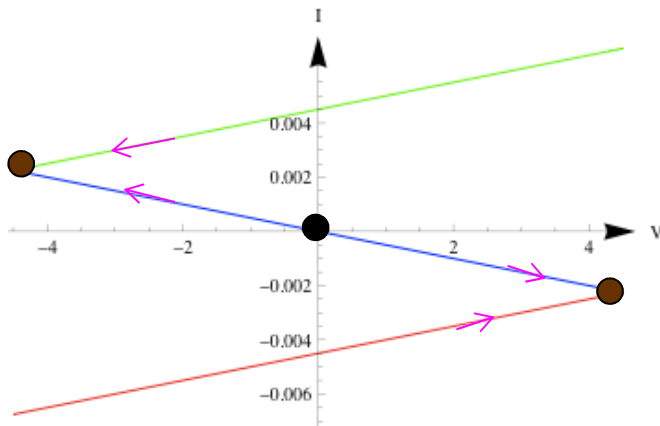

The period is 2x the switching time t_s :

$$4.5 = 9 - 13.5e^{-\left(t_s/R_f C\right)}$$


$$\text{Period} = 2t_s = 2\ln(3)R_f C$$

Finding the duty cycle

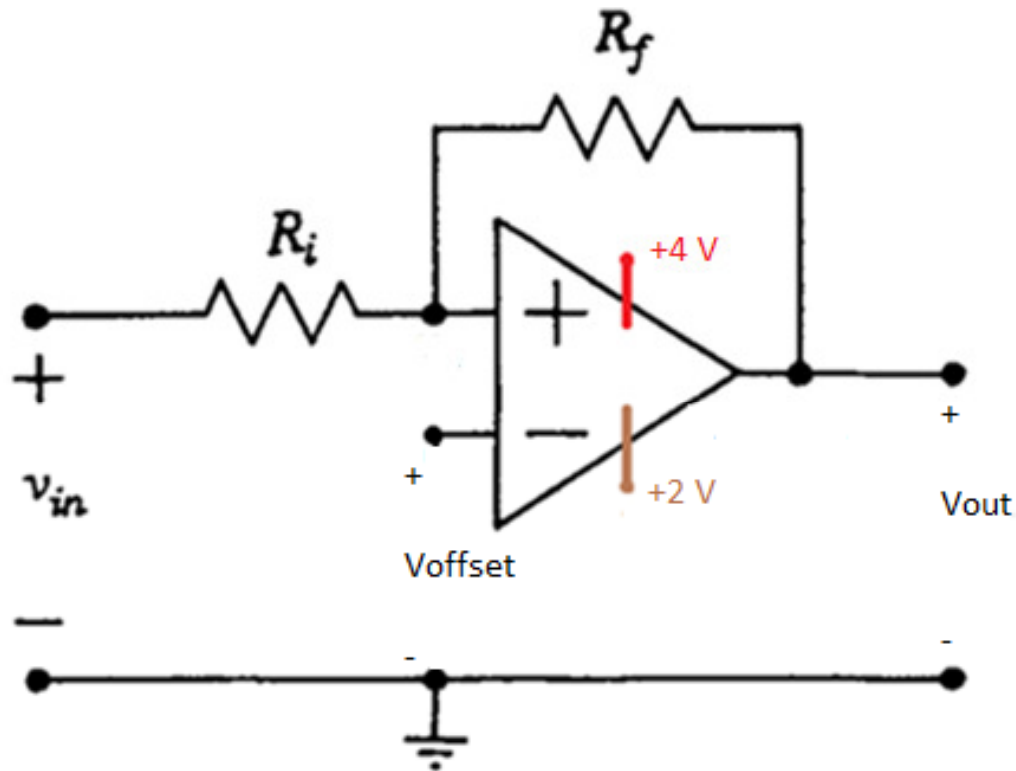1. Recall (from last lecture): $v_p = \frac{R_2}{R_1 + R_2} v_0$
2. Circuit switches state when (positive saturation): $v_p > v_n$
3. In other words : $V < \frac{R_2}{R_1 + R_2} V_{dd}$
4. Hence, duty cycle is controlled by V_{dd} and V_{ss}

Conclusion

Sketch V_{out} vs V_{in} for the circuit below, for a constant V_{offset} .



Questions??