

Simplest¹ (LCM) Chaotic Circuit

Vellore Institute of Technology

August 27th 2012

Bharathwaj “Bart” Muthuswamy

Assistant Professor of Electrical Engineering

Milwaukee School of Engineering

muthuswamy@msoe.edu

<http://www.harpgroup.org/muthuswamy/>

BS (2002), MS (2005) and PhD (2009) from the University of California, Berkeley

PhD Advisor: Dr. Leon O. Chua (co-advised by Dr. Pravin P. Varaiya)




What do I work on?

Nonlinear Dynamical Systems and Embedded Systems

- Applications and Mathematical properties of the LCM chaotic circuit
 - Number Theory (Bharathidasan University, Tiruchy, India)
 - Local activity (University of Western Australia, Perth, Australia)
 - Flow manifolds (I.U.T. de Toulon, La Garde Cedex, France)
- Applications of Chaotic Delay Differential Equations using Field Programmable Gate Arrays (University Putra Malaysia, Malaysia)
- Pattern Recognition Using Cellular Neural Networks (University of California, Berkeley, USA)
- Gait generation using nonlinear dynamics for children with Cerebral Palsy* (Medical College of Wisconsin, Wauwutosa, USA)
- Memristive behavior in superconductors (University of California, Berkeley, USA; Vellore Institute of Technology*, Vellore, India)


Education

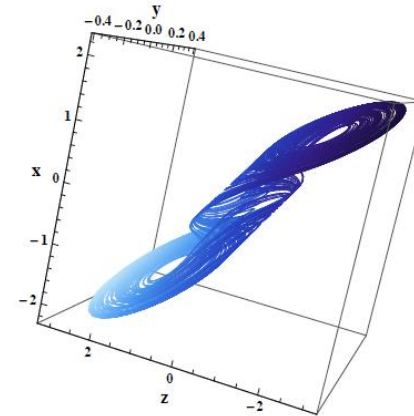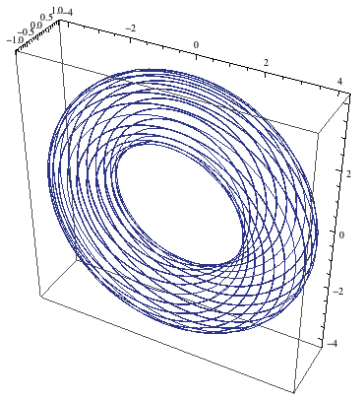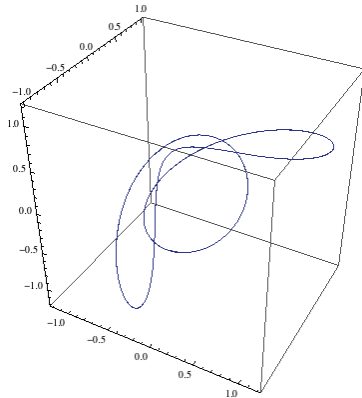- edX program (University of California, Berkeley; Massachusetts Institute of Technology; Harvard University, USA)
- Nonlinear Dynamics at the undergraduate level (with folks from all over the world ☺)



Goal of This Talk

Obtain chaos in the circuit [5] below:

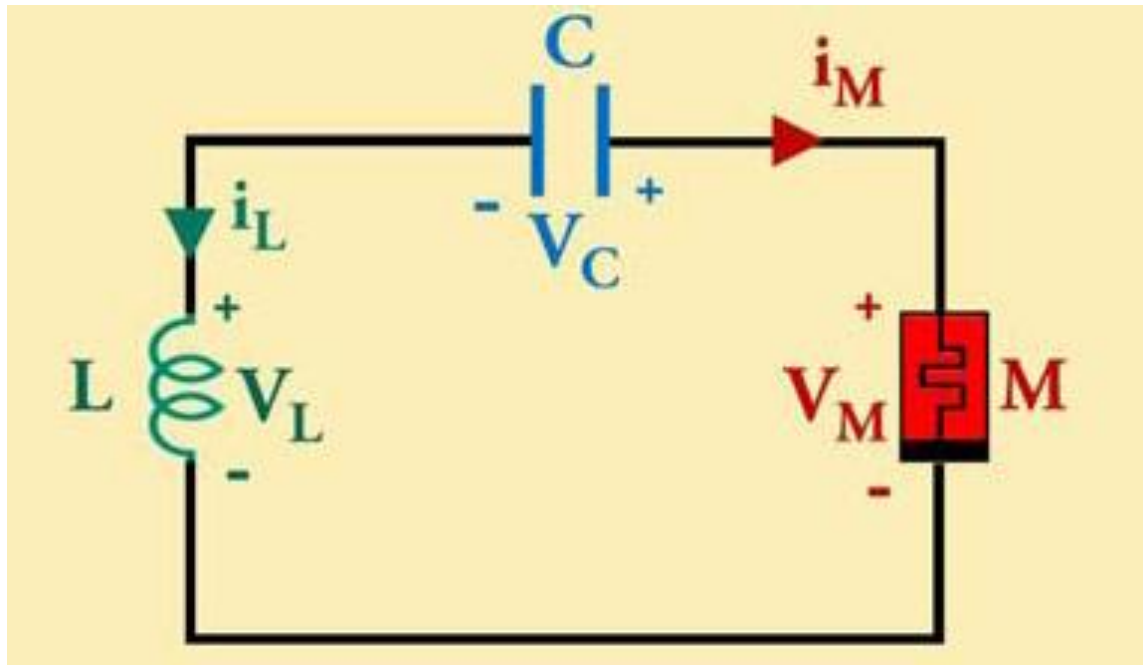

Outline

- I. Prerequisites for understanding this talk:
 1. First course in circuit theory
 2. First course in differential equations
- II. Background
 1. Introduction to Chaos
 2. The fundamental circuit elements
- III. The Memristor
 1. Properties of the memristor
 2. Hewlett-Packard's Memristor
 3. Memristive Devices
- IV. Simplest Chaotic Circuit
 1. Derivation of Circuit Equations
 2. Physical realization of the memristor
 3. Attractors from the circuit
 4. Rigorous Mathematical Analysis
- V. Conclusions, Future work and References

Introduction to chaos

- “Birth” of Chaos: Lorenz Attractor [6]
 - Edward Lorenz introduced the following nonlinear system of differential equations as a crude model of weather in 1963:


$$\begin{aligned}\dot{\mathbf{x}} &= -\sigma \cdot \mathbf{x} + \sigma \cdot \mathbf{y} \\ \dot{\mathbf{y}} &= \rho \cdot \mathbf{x} - \mathbf{y} - \mathbf{x} \cdot \mathbf{z} \\ \dot{\mathbf{z}} &= -\beta \cdot \mathbf{z} + \mathbf{x} \cdot \mathbf{y}\end{aligned}\quad (1)$$

Parameters: $\sigma = 10, \rho = 28, \beta = \frac{8}{3}$

ICs: $x_0 = 10, y_0 = 20, z_0 = 30,$

Simulation time: 100 seconds

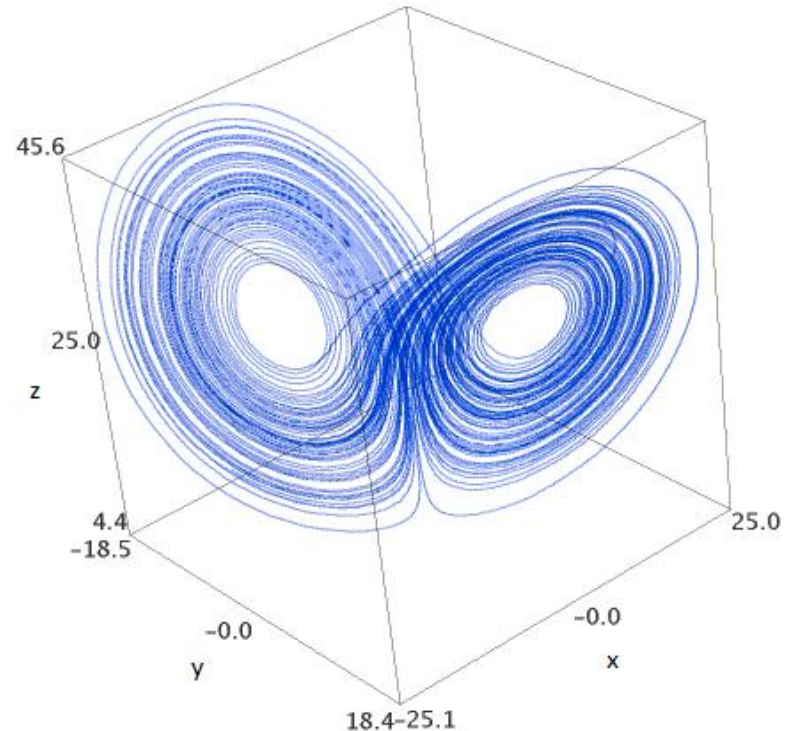
- Lorenz discovered that model dynamics were extremely sensitive to initial conditions and the trajectories were aperiodic but bounded.
- But, does chaos exist *physically*? Answer is: YES. For example, chaotic circuits by Sprott [7].



Outline

- I. Prerequisites for understanding this talk:
 1. First course in circuit theory
 2. First course in differential equations
- II. Background
 1. Introduction to Chaos
 2. The fundamental circuit elements
- III. The Memristor
 1. Properties of the Memristor
 2. Hewlett-Packard's Memristor
 3. Memristive Devices
- IV. Simplest Chaotic Circuit
 1. Derivation of Circuit Equations
 2. Physical realization of the memristor
 3. Attractors from the circuit
 4. Rigorous Mathematical Analysis
- V. Conclusions, Future work and References


The Fundamental Circuit Elements

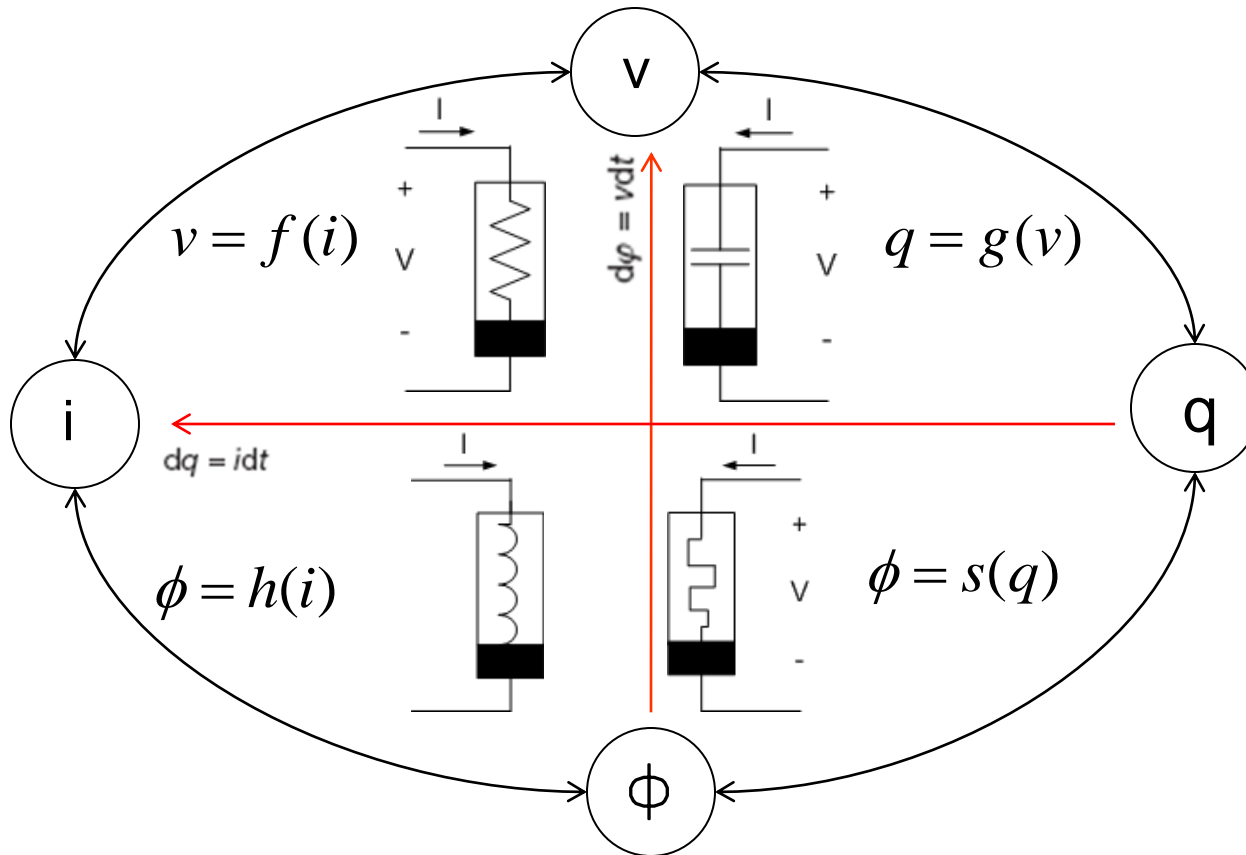

Memristors were first postulated by Leon. O Chua in 1971 [2]

Properties of the Memristor [2]

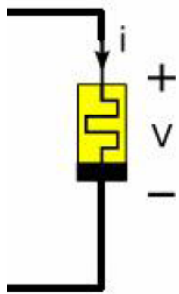Circuit symbol: A memristor defines a *relation* of the form: $g(\phi, q) = 0$ (2)




If g is a single-valued function of charge (flux), then the memristor is charge-controlled (flux-controlled)

Memristor i-v relationship:

$M(q(t))$ is the incremental memristance
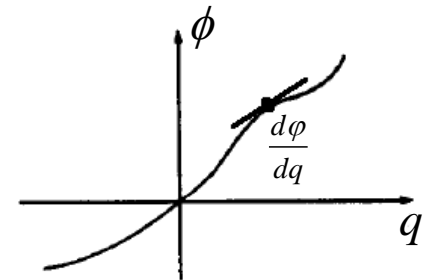
$$v(t) \triangleq \frac{d\phi}{dt} = \frac{d\phi}{dq} \frac{dq}{dt} \triangleq M(q(t))i(t) \quad (3)$$



Q1: Why is the memristor called “memory resistor”?



Because of the definition of memristance: $v(t) = M(q(t))i(t) = M\left(\int_{-\infty}^t i(\tau)\right)i(t)$

Q2: Why is the memristor not relevant in linear circuit theory?



1. If $M(q(t))$ is a constant: $v(t) = M(q(t))i(t) = Mi(t) = Ri(t)$



2. Principle of superposition is not* applicable:

$$M\left(\int_{-\infty}^t (i_1 + i_2)(\tau)\right)(i_1 + i_2)(t) = M\left(\int_{-\infty}^t (i_1)(\tau) + \int_{-\infty}^t (i_2)(\tau)\right)(i_1 + i_2)(t) \neq M\left(\int_{-\infty}^t (i_1)(\tau)\right)i_1(t) + M\left(\int_{-\infty}^t (i_2)(\tau)\right)i_2(t)$$

Outline

- I. Prerequisites for understanding this talk:
 1. First course in circuit theory
 2. First course in differential equations
- II. Background
 1. Introduction to Chaos
 2. The fundamental circuit elements
- III. The Memristor
 1. Properties of the Memristor
 2. Hewlett-Packard's Memristor
 3. Memristive Devices
- IV. Simplest Chaotic Circuit
 1. Derivation of Circuit Equations
 2. Physical realization of the memristor
 3. Attractors from the circuit
 4. Rigorous Mathematical Analysis
- V. Conclusions, Future work and References

Hewlett-Packard's memristor [9]

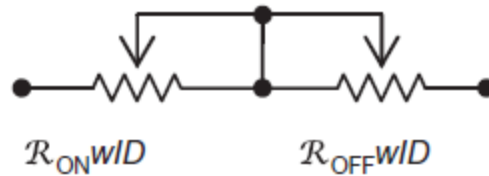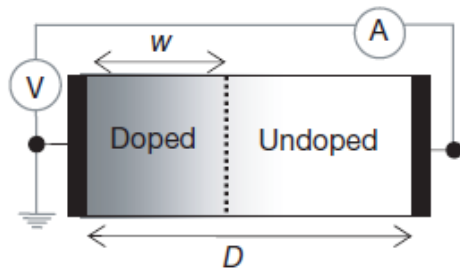

Undoped:




Doped:



$$v(t) = \left(\mathcal{R}_{ON} \frac{w(t)}{D} + \mathcal{R}_{OFF} \left(1 - \frac{w(t)}{D} \right) \right) i(t)$$

$$\frac{dw(t)}{dt} = \mu_V \frac{\mathcal{R}_{ON}}{D} i(t)$$
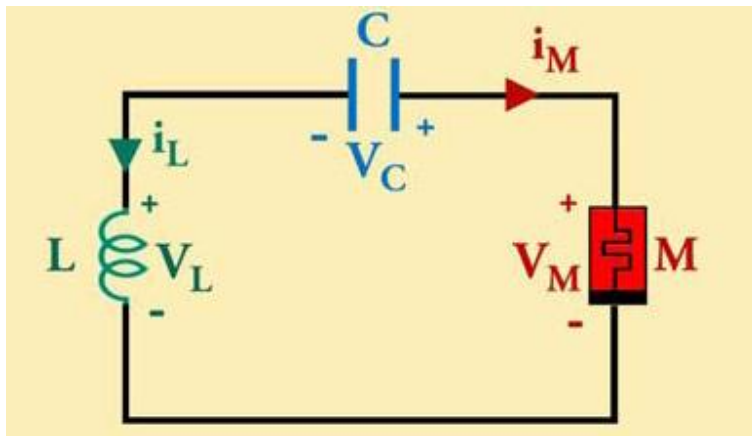
$$\xrightarrow{\mathcal{R}_{ON} \ll \mathcal{R}_{OFF}} M(q) = \mathcal{R}_{OFF} \left(1 - \frac{\mu_V \mathcal{R}_{ON}}{D^2} q(t) \right)$$



Circuit equations:

$$\dot{v}_C = \frac{i_L}{C}$$

$$\dot{q}_M = -i_L \xrightarrow{x \triangleq v_C, z \triangleq q_M, y \triangleq i_L}$$

System equations:


$$\dot{x} = \frac{y}{C}$$

$$\dot{z} = -y$$

$$\dot{y} = \frac{-1}{L} (x + M(z)y) \quad (5)$$

$$v_L + v_C = v_M \Rightarrow L \frac{di_L}{dt} = -v_C + M(q_M) i_M \Rightarrow i'_L = \frac{-1}{L} (v_C + M(q_M) i_L)$$

Memristive Devices [3]

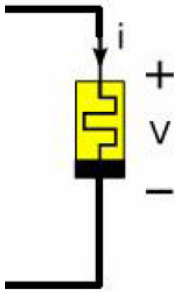

$$\begin{aligned} v &\triangleq R(z, i)i \\ \dot{z} &= f(z, i) \end{aligned} \quad (6)$$


$$\xrightarrow{z \triangleq q, R(z, i) \triangleq M(q)}$$

$$\begin{aligned} v &\triangleq M(q)i \\ \dot{q} &= i \end{aligned}$$

The functions R and f are defined as:

$$R : \mathbb{R}^1 \times \mathbb{R} \rightarrow \mathbb{R}$$
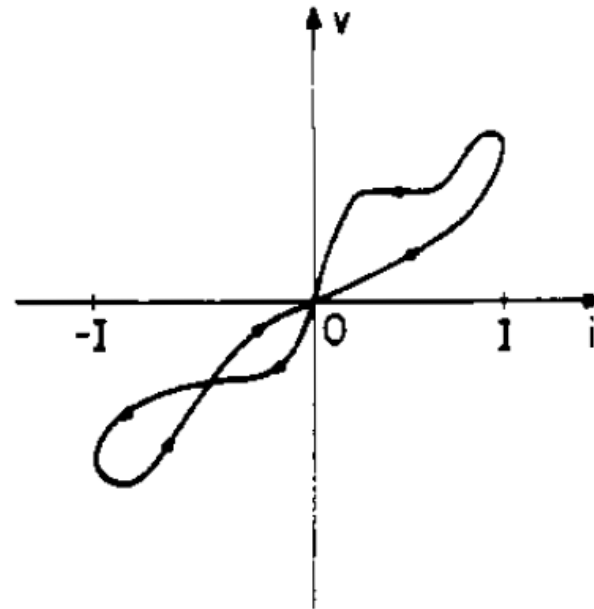
$$f : \mathbb{R}^1 \times \mathbb{R} \rightarrow \mathbb{R}^1$$




Outline

- I. Prerequisites for understanding this talk:
 1. First course in circuit theory
 2. First course in differential equations
- II. Background
 1. Introduction to Chaos
 2. The fundamental circuit elements
- III. The Memristor
 1. Properties of the Memristor
 2. Hewlett-Packard's Memristor
 3. Memristive Devices
- IV. Simplest Chaotic Circuit
 1. Derivation of Circuit Equations
 2. Physical realization of the memristor
 3. Attractors from the circuit
 4. Rigorous Mathematical Analysis
- V. Conclusions, Future work and References

Derivation of Circuit Equations [5]

$$v_M \triangleq R(z, i_M) i_M$$

$$\dot{z} = f(z, i_M)$$

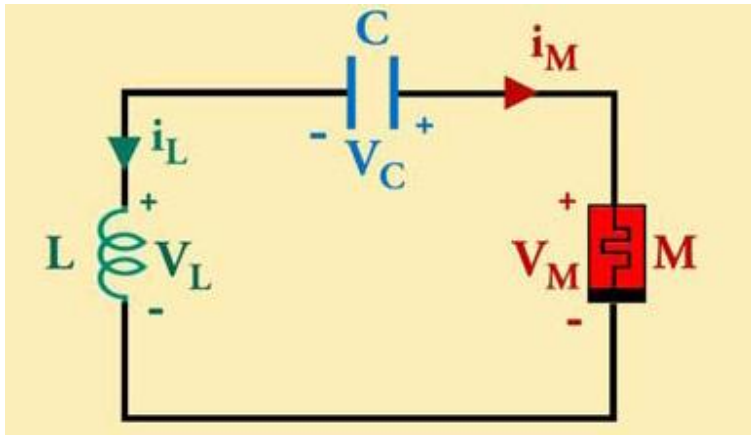

Circuit equations:

$$\dot{v}_c = \frac{i_L}{C}$$

$$i'_L = \frac{-1}{L} (v_C + R(z, i_L) i_L)$$

$$\dot{z} \triangleq f(z, i_L)$$

System equations:

$$\begin{matrix} x \triangleq v_c, y \triangleq i_L \\ \dot{x} = \frac{y}{C} \\ \dot{y} = \frac{-1}{L} (x + R(z, y) y) \\ \dot{z} = f(z, y) \end{matrix} \quad (7)$$

Specifically:

$$\dot{x} = \frac{y}{C}$$

$$\dot{y} = \frac{-1}{L} (x + \beta(z^2 - 1)y) \quad (8)$$

$$\dot{z} = -y - \alpha z + yz$$

Parameters:

$$\begin{matrix} \longrightarrow \\ C = 1, L = 3 \\ \beta = \frac{3}{2}, \alpha = \frac{3}{5} \end{matrix}$$

$$\dot{x} = y$$


$$\dot{y} = \frac{-x}{3} - \frac{z^2 y}{2} + \frac{y}{2} \quad (9)$$

$$\dot{z} = -y - 0.6z + yz$$


Outline

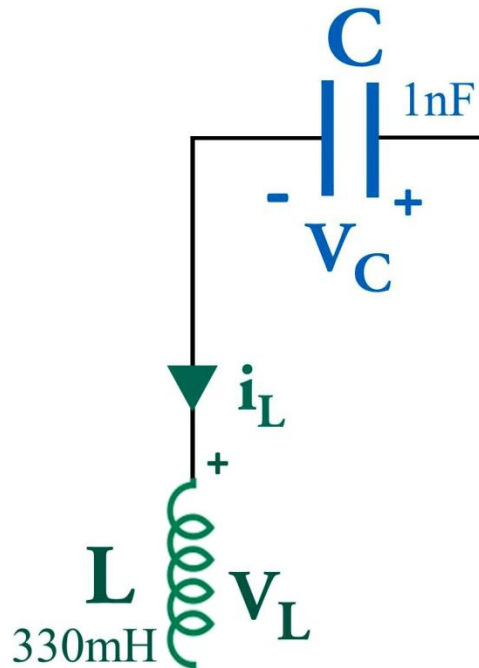- I. Prerequisites for understanding this talk:
 1. First course in circuit theory
 2. First course in differential equations
- II. Background
 1. Introduction to Chaos
 2. The fundamental circuit elements
- III. The Memristor
 1. Properties of the Memristor
 2. Hewlett-Packard's Memristor
 3. Memristive Devices
- IV. Simplest Chaotic Circuit
 1. Derivation of Circuit Equations
 2. Physical realization of the memristor
 3. Attractors from the circuit
 4. Rigorous Mathematical Analysis
- V. Conclusions, Future work and References

Physical Realization of the Memristor [5]






Memristor

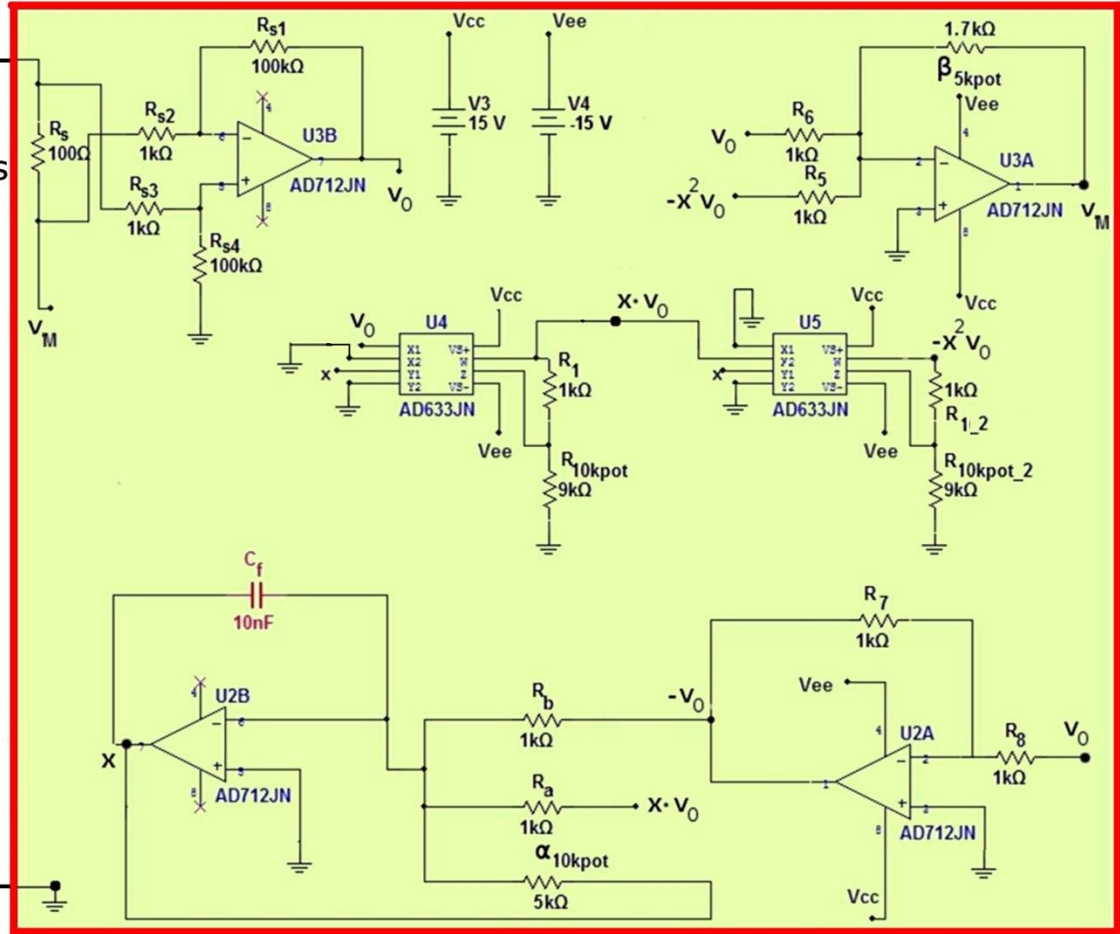

Outline

- I. Prerequisites for understanding this talk:
 1. First course in circuit theory
 2. First course in differential equations
- II. Background
 1. Introduction to Chaos
 2. The fundamental circuit elements
- III. The Memristor
 1. Properties of the Memristor
 2. Hewlett-Packard's Memristor
 3. Memristive Devices
- IV. Simplest Chaotic Circuit
 1. Derivation of Circuit Equations
 2. Physical realization of the memristor
 3. Attractors from the circuit
 4. Rigorous Mathematical Analysis
- V. Conclusions, Future work and References

Attractors from the Circuit [5]

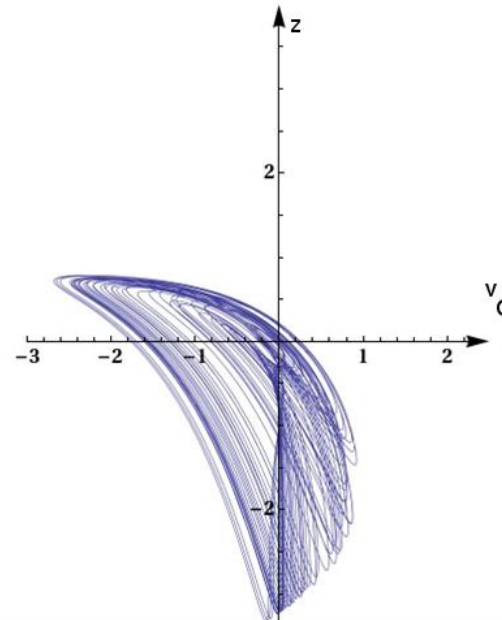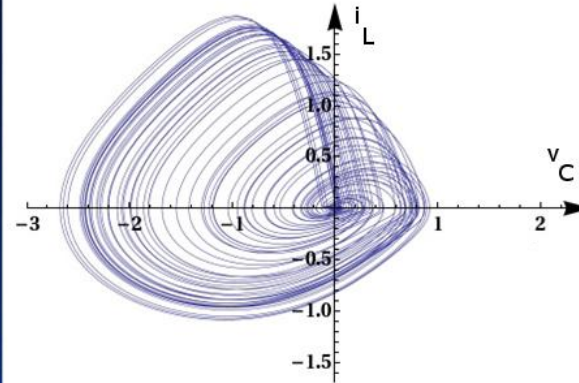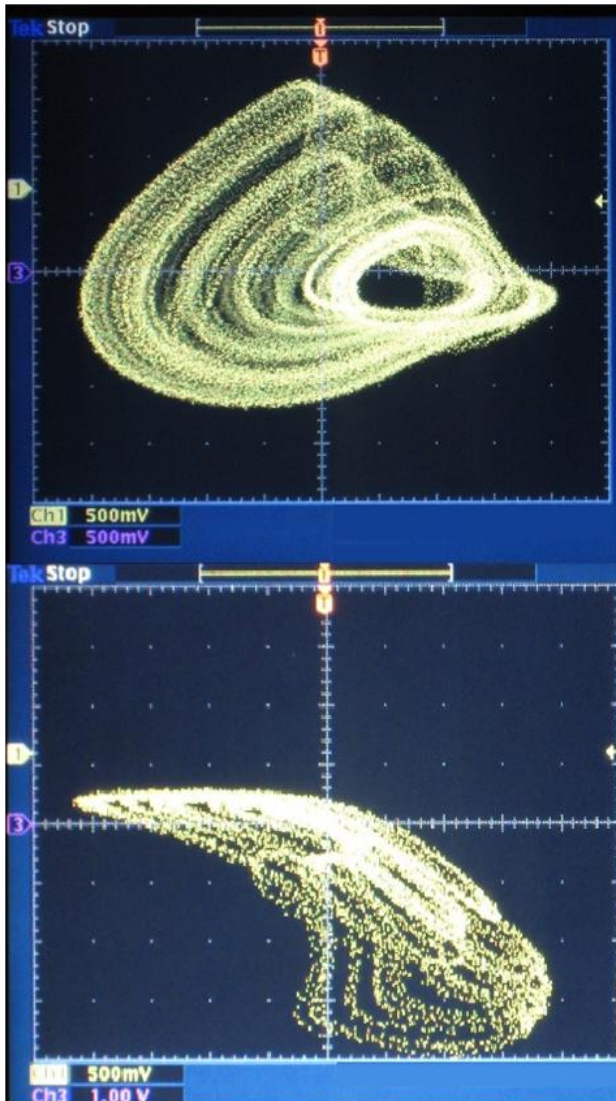

Outline

- I. Prerequisites for understanding this talk:
 1. First course in circuit theory
 2. First course in differential equations
- II. Background
 1. Introduction to Chaos
 2. The fundamental circuit elements
- III. The Memristor
 1. Properties of the Memristor
 2. Hewlett-Packard's Memristor
 3. Memristive Devices
- IV. Simplest Chaotic Circuit
 1. Derivation of Circuit Equations
 2. Physical realization of the memristor
 3. Attractors from the circuit
 4. Rigorous Mathematical Analysis
- V. Conclusions, Future work and References




Rigorous Mathematical Analysis

Paper by Ginoux et. al. "Topological Analysis of Chaotic Solution of Three-Element Memristive Circuit". International Journal of Bifurcation and Chaos, Vol. 20, No. 11., pp. 3819 – 3829, Nov. 2010.

$$\dot{x} = y$$

$$\dot{y} = -\frac{x}{3} + \frac{y}{2} - \frac{yz^2}{2}$$

$$\dot{z} = y - \alpha z - yz$$

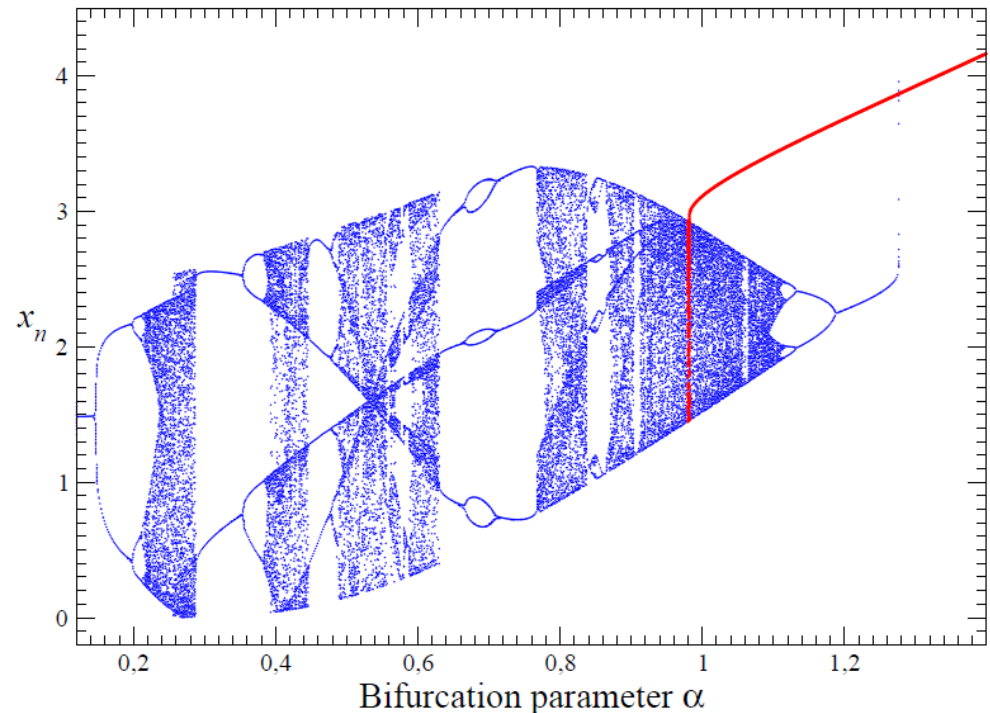

Outline

- I. Prerequisites for understanding this talk:
 1. First course in circuit theory
 2. First course in differential equations
- II. Background
 1. Introduction to Chaos
 2. The fundamental circuit elements
- III. The Memristor
 1. Properties of the Memristor
 2. Hewlett-Packard's Memristor
 3. Memristive Devices
- IV. Simplest Chaotic Circuit
 1. Derivation of Circuit Equations
 2. Physical realization of the memristor
 3. Attractors from the circuit
 4. Rigorous Mathematical Analysis
- V. Conclusions, Future work and References

Conclusions and Future Work

I. Conclusions:

1. We obtained a circuit that uses only *three fundamental circuit elements (only one active)* to obtain chaos.
2. We can pick our choice of nonlinearity, we discussed one particular choice.

II. Future work:

1. **Physical memristor from the Josephson Junction**

References

1. Alligood, K. T., Sauer, T. and Yorke, J. A. *Chaos: An Introduction to Dynamical Systems*. Springer, 1997.
2. Chua, L. O. "Memristor-The Missing Circuit Element". *IEEE Transactions on Circuit Theory*, Vol. CT-18, No. 5, pp. 507- 519. September 1971.
3. Chua, L. O. and Kang, S. M. "Memristive Devices and Systems". *Proceedings of the IEEE*, Vol. 64, No. 2, pp. 209- 223. February 1976.
4. Hirsch, M. W., Smale S. and Devaney, R. *Differential Equations, Dynamical Systems and An Introduction To Chaos*. 2nd Edition, Elsevier, 2004.
5. Muthuswamy, B. and Chua, L. O. "Simplest Chaotic Circuit". *International Journal of Bifurcation and Chaos*, vol. 20, No. 5, pp. 1567-1580. May 2010.
6. Lorenz, E. N. "Deterministic Nonperiodic Flow". *Journal of Atmospheric Sciences*, vol. 20, pp/ 130-141, 1963.
7. Sprott, J. C. "Simple Chaotic Systems and Circuits". *American Journal of Physics*, vol. 68, pp. 758-763, 2000.
8. Strogatz, S. H. *Nonlinear Dynamics and Chaos*. Addison-Wesley, 1994.
9. Strukov, D. B., Snider, G. S., Steward, D. R. and Williams, S. R. "The missing memristor found". *Nature*, vol. 453, pp. 81-83, 1st May 2008.

Questions?