

# Non-ideal and Ideal Memristors : The Fourth Fundamental Circuit Element

Institute of Advanced Studies  
University of Western Australia

June 9<sup>th</sup> 2014

Bharathwaj “Bart” Muthuswamy  
Assistant Professor of Electrical Engineering  
Milwaukee School of Engineering

[muthuswamy@msoe.edu](mailto:muthuswamy@msoe.edu)

<http://www.harpgroup.org/muthuswamy/>

BS (2002), MS (2005) and PhD (2009) from the University of California, Berkeley  
PhD Advisor: Dr. Leon O. Chua (co-advised by Dr. Pravin P. Varaiya)






# What do I work on?

## Nonlinear Dynamical Systems and Embedded Systems

- Physical Memristors: discharge tubes, PN junctions and Josephson Junctions  
(MSOE; IIT Chennai; University of Western Australia, Perth, Australia; Vellore Institute of Technology, Vellore, India)
- Applications and Mathematical properties of the Muthuswamy-Chua system  
(MSOE; University of Western Australia, Perth, Australia)
- Applications of Chaotic Delay Differential Equations using Field Programmable Gate Arrays (FPGAs)  
(MSOE; Vellore Institute of Technology; University Putra Malaysia, Malaysia )
- Pattern Recognition Using Cellular Neural Networks on FPGAs  
(MSOE; Altera Corporation)
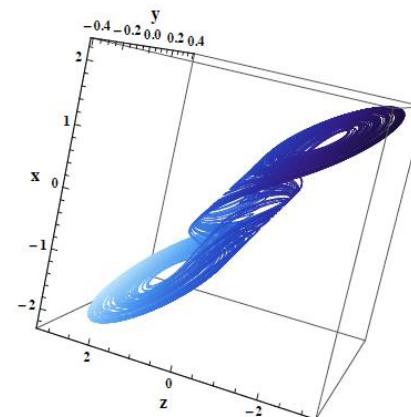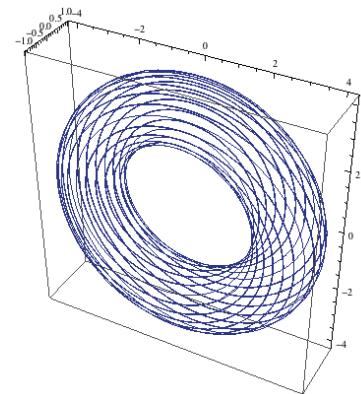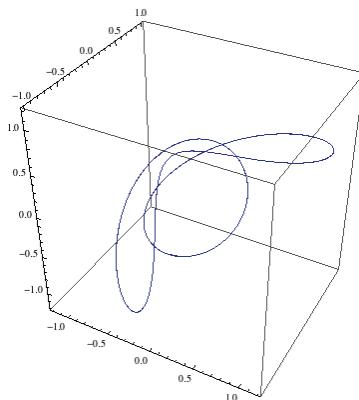
## Education

- Nonlinear Dynamics at the undergraduate level (with folks from all over the world ☺ )



# Primary Goal of this Talk

Discuss properties [2], [4] of physical  
memristors [4], [3], [6], [9], [10]

# Outline

## I. Background

1. The Fundamental Circuit Elements
2. The Art and Science of Device Modeling

## II. A “Familiar” Example – The junction diode

1. Circuit Model

## III. The Memristor


1. Properties of the Memristor
2. Memristive Devices
3. Memristor Emulator

## IV. Physical Memristors

1. Non-ideal versus Ideal Memristors
2. Non-ideal Memristors:
  - a. Discharge tube
  - b. Junction diode
3. Ideal memristor:
  - a. Josephson junction

## V. Conclusions, Current (future) work and References

# The Fundamental Circuit Elements

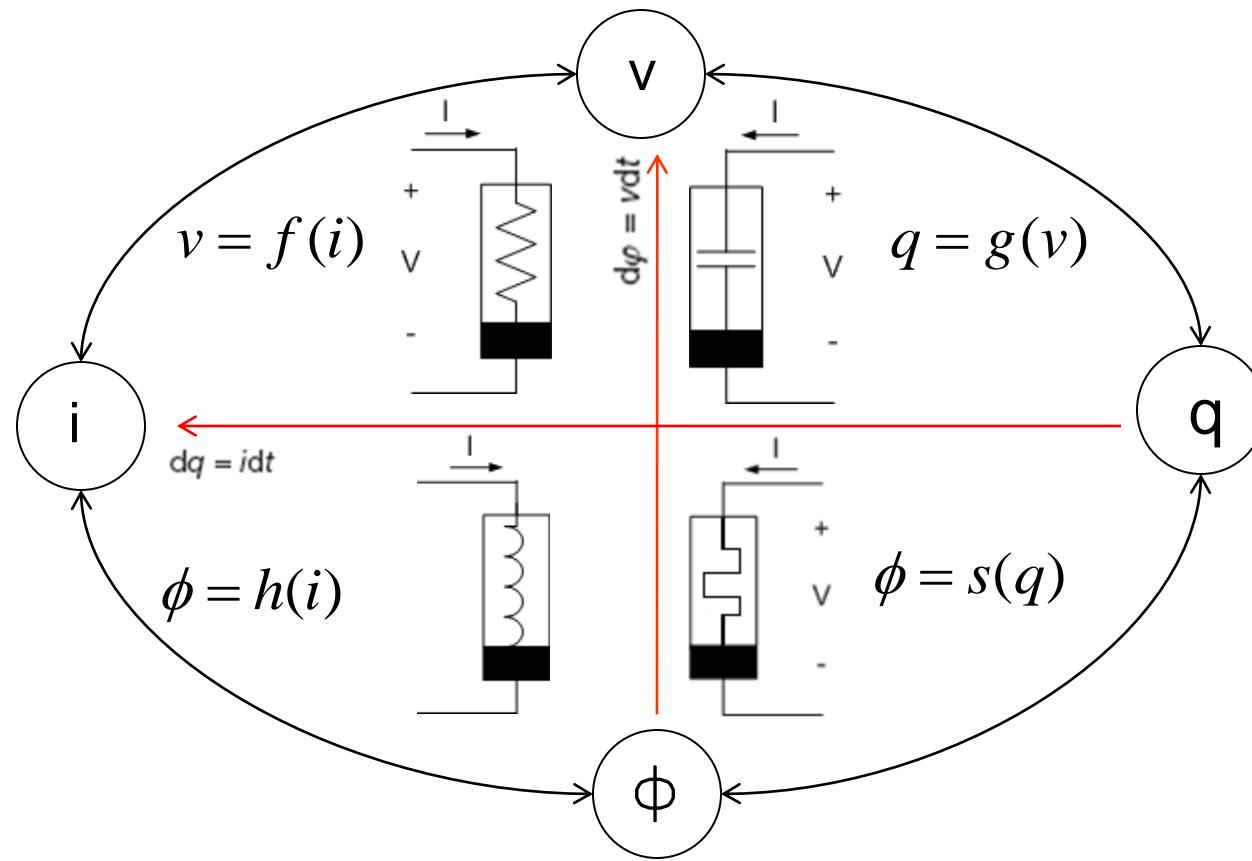

Memristors were first postulated by Leon. O Chua in 1971 [2]. In 2008, researchers at HP claimed to have found the “missing” memristor [11].

# The Fundamental Circuit Elements (contd.)

But Paul Penfield from an MIT 1973 technical report [10], states:

Thompson also shows an equivalent circuit that has a parasitic loss element denoted  $G(v)$  to represent, among other things, tunneling electron current. A somewhat more accurate model<sup>4</sup> for this loss is a resistor whose value depends not upon the voltage but rather upon the superconducting phase, i. e., upon the integral of the voltage. Chua<sup>5</sup> has discussed this model, and given it the name "memristor." In particular, Chua has given the form of the frequency-power formulas for memristors, and they are different from the Manley-Rowe equations, and from the formulas for nonlinear resistors.

# The Science and Art of Device Modeling

We first have to understand that a circuit model is not an equivalent circuit of a device since no physical device can be exactly mimicked by a circuit or mathematical model [9]. In fact, depending on the application (e.g., frequency of operation), a given device may have many distinct physical models [9]. There is no "best model" for all occasions. The best model in a given situation is the simplest model capable of yielding realistic solutions [9]. Thus device modeling is both an art (physical device equation formulation) and science (nonlinear network synthesis).

# Outline

## I. Background

1. The Fundamental Circuit Elements
2. The Art and Science of Device Modeling

## II. A “Familiar” Example – The junction diode

1. Circuit Model

## III. The Memristor


1. Properties of the Memristor
2. Memristive Devices
3. Memristor Emulator

## IV. Physical Memristors

1. Non-ideal versus Ideal Memristors
2. Non-ideal Memristors:
  - a. Discharge tube
  - b. Junction diode
3. Ideal memristor:
  - a. Josephson junction

## V. Conclusions, Current (future) work and References
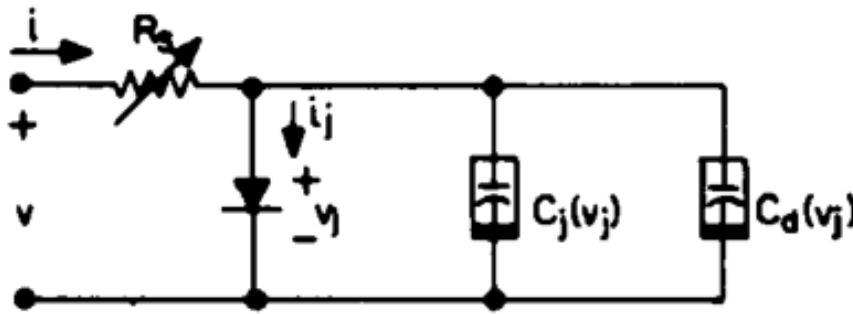
# A “Familiar” Example – The junction diode: Circuit Model [3]



Bonna-Horelick Model

$$R_s = R_0 f(i_j) \quad \text{where:}$$
$$f(i_j) \triangleq 1 - \frac{1}{X_n} \ln \frac{1 + K_r i_j}{1 + K_r i_j e^{-X_n}}$$

$R_0$ ,  $X_n$  and  $K_r$  are diode parameters

# Outline

## I. Background

1. The Fundamental Circuit Elements
2. The Art and Science of Device Modeling

## II. A “Familiar” Example – The junction diode

1. Circuit Model

## III. The Memristor

1. Properties of the Memristor
2. Memristive Devices
3. Memristor Emulator


## IV. Physical Memristors

1. Non-ideal versus Ideal Memristors
2. Non-ideal Memristors:
  - a. Discharge tube
  - b. Junction diode
3. Ideal memristor:
  - a. Josephson junction

## V. Conclusions, Current (future) work and References
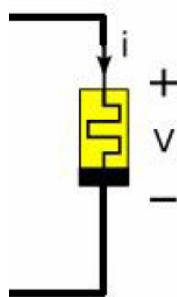
# Properties of the Memristor [2] [4]

Circuit symbol: A memristor defines a *relation* of the form:  $g(\phi, q) = 0$  (1)




If  $g$  is a single-valued function of charge (flux), then the memristor is charge-controlled (flux-controlled)

Memristor i-v relationship:

$M(q(t))$  is the incremental memristance

$$v(t) \triangleq \frac{d\phi}{dt} = \frac{d\phi}{dq} \frac{dq}{dt} \triangleq M(q(t))i(t) \quad (2)$$

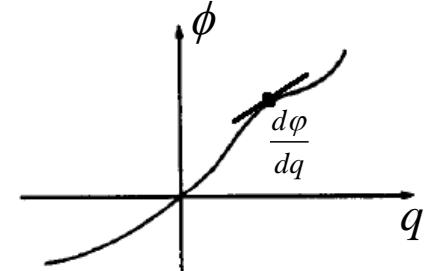Q1: Why is the memristor called “memory resistor”?



Because of the definition of memristance:  $v(t) = M(q(t))i(t) = M \left( \int_{-\infty}^t i(\tau) d\tau \right) i(t) \quad (3)$


Q2: Why is the memristor not relevant in linear circuit theory?

1. If  $M(q(t))$  is a constant:  $v(t) = M(q(t))i(t) = Mi(t) = Ri(t) \quad (4)$

2. Principle of superposition is not\* applicable. Proof:

$$M \left( \int_{-\infty}^t (i_1 + i_2)(\tau) d\tau \right) (i_1 + i_2)(t) = M \left( \int_{-\infty}^t i_1(\tau) d\tau + \int_{-\infty}^t i_2(\tau) d\tau \right) (i_1 + i_2)(t) \neq M \left( \int_{-\infty}^t i_1(\tau) d\tau \right) i_1(t) + M \left( \int_{-\infty}^t i_2(\tau) d\tau \right) i_2(t)$$

# Memristive Devices [4]

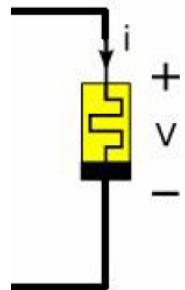


$$\begin{aligned}v &\triangleq R(\vec{z}, i)i \\ \dot{\vec{z}} &= f(\vec{z}, i)\end{aligned}\quad (5)$$

$$\xrightarrow{\vec{z} \triangleq q, R(\vec{z}, i) \triangleq M(q)} \begin{aligned}v &\triangleq M(q)i \\ \dot{q} &= i\end{aligned}\quad (6)$$

The functions  $R$  and  $f$  are defined as:


$$R : \mathbb{R}^n \times \mathbb{R} \rightarrow \mathbb{R}$$
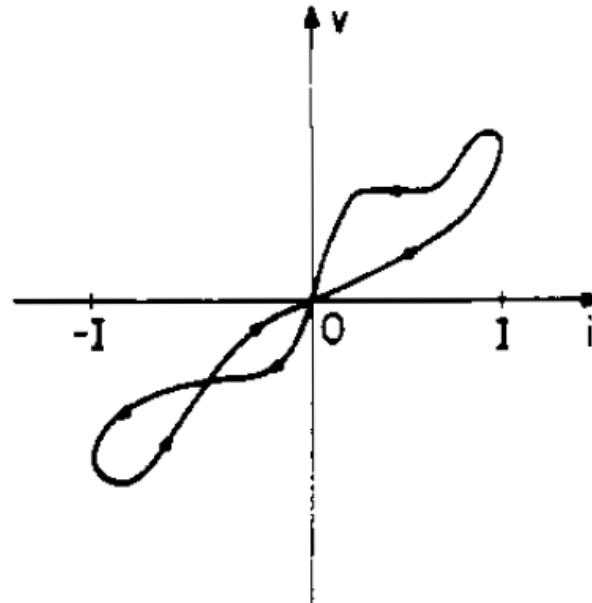
$$f : \mathbb{R}^n \times \mathbb{R} \rightarrow \mathbb{R}^n$$




In Eq. (5),  $R(\vec{z}, i) \not\rightarrow \infty$

# Memristor Emulation [8]

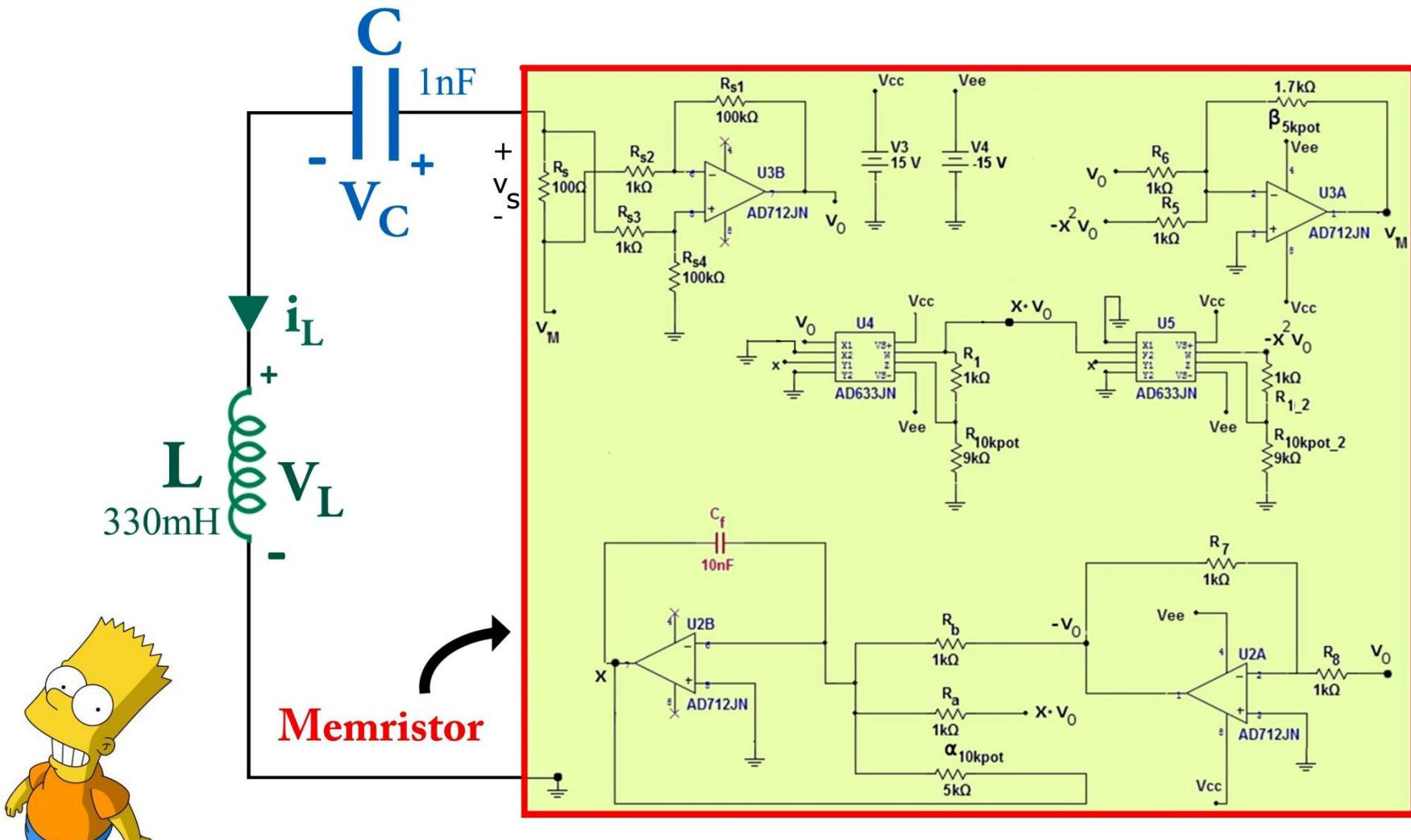
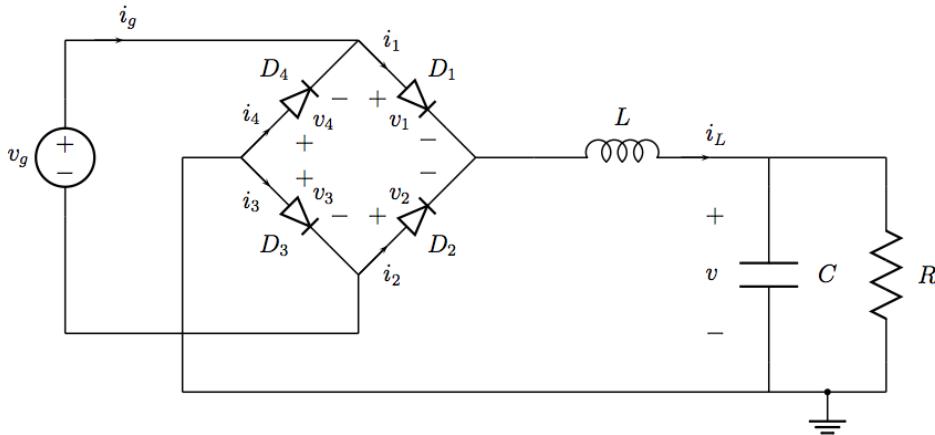
# Memristor Emulation : Passive Elements only [5]



$$v_1 = nV_T \ln \left( \frac{i_L + 2I_S}{2I_S \exp \left( -\frac{v_g}{2nV_T} \right) \cosh \left( \frac{v_g}{2nV_T} \right)} \right) \quad (7)$$

$$i_g = (i_L + 2I_S) \tanh \left( \frac{v_g}{2nV_T} \right) \quad (8)$$

$$\begin{aligned} \frac{d\mathbf{x}}{dt} &= f(\mathbf{x}, u, t) \\ y &= g(\mathbf{x}, u, t)u \end{aligned} \quad (9)$$

←

$$\begin{aligned} x_1 &= v (V_T)^{-1} \\ x_2 &= i_L (I_S)^{-1} \\ u &= v_g (V_T)^{-1} \\ y &= i_g (I_S)^{-1} \\ \tau &= t (t_0)^{-1} \\ t_0 &= 2\pi (\omega_0)^{-1} \\ \omega_0 &= [(LC)^{-1} - (RC)]^{\frac{1}{2}} \end{aligned}$$


$$f(\mathbf{x}, u, t) = \begin{bmatrix} \beta(x_2 - \alpha x_1) \\ \gamma \left( u - x_1 - 2 \ln \left( \frac{x_2 + 2}{2 \exp(-\frac{u}{2n}) \cosh(\frac{u}{2n})} \right) \right) \end{bmatrix} \quad (10)$$

$$g(\mathbf{x}, u, t) = (x_2 + 2) \frac{\sum_{m=0}^{\infty} \frac{(\frac{u}{2n})^{2m}}{(2m+1)!}}{\sum_{m=0}^{\infty} \frac{(\frac{u}{2n})^{2m}}{(2m)!}}, \quad (11)$$

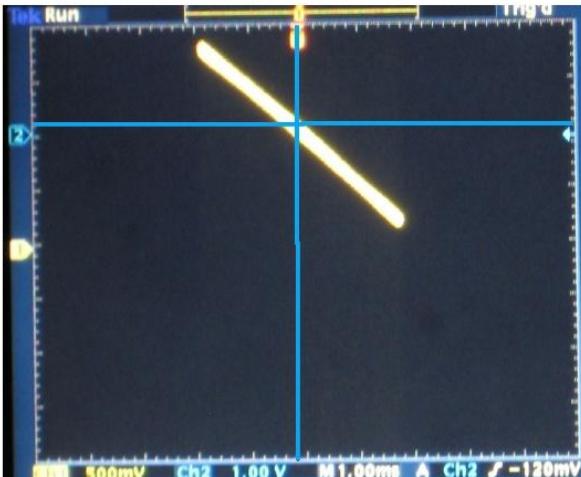
# Memristor Emulators – Pinched Hysteresis Loops [8] [5]



From [3], pinched-hysteresis for 3 kHz sinusoidal input



From [3], pinched-hysteresis for 35 kHz sinusoidal input

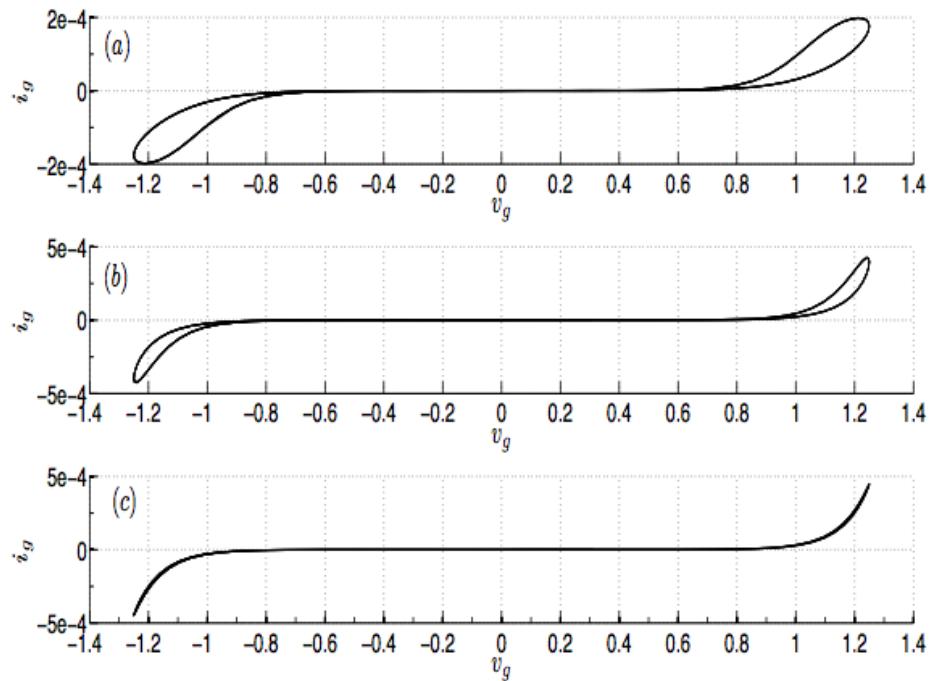

**Fig. 3** Current-voltage characteristics observed in numerical simulations of the mathematical model of the proposed circuit for a sine-wave input with  $f$  set to 10 (plot (a)), 100 (plot (b)) and 1000 Hz (plot (c)).

From [4]

# Outline

## I. Background

1. The Fundamental Circuit Elements
2. The Art and Science of Device Modeling

## II. A “Familiar” Example – The junction diode

1. Circuit Model

## III. The Memristor

1. Properties of the Memristor
2. Memristive Devices
3. Memristor Emulator

## IV. Physical Memristors

1. Non-ideal versus Ideal Memristors
2. Non-ideal Memristors:
  - a. Discharge tube
  - b. Junction diode
3. Ideal memristor:
  - a. Josephson junction

## V. Conclusions, Current (future) work and References

# Non-ideal versus Ideal Memristors

Definition:

A memristor that establishes a relation between charge and flux is an ideal memristor. Any other memristor (memristive device) is non-ideal.

# Non-ideal Memristor : Discharge Tube [9]

$$v = M(n)i$$

$$\dot{n} = -\beta n + \alpha M(n)i^2 \quad (12)$$

$$M(n) \triangleq \frac{F}{n} \quad (13)$$

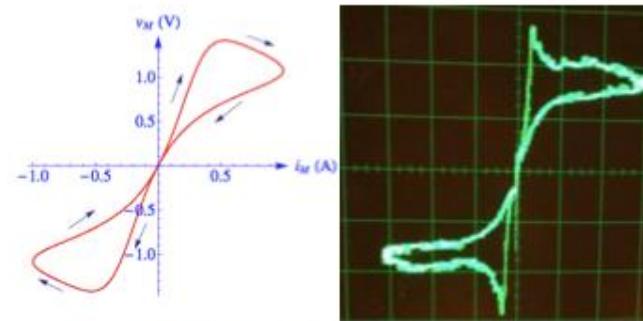
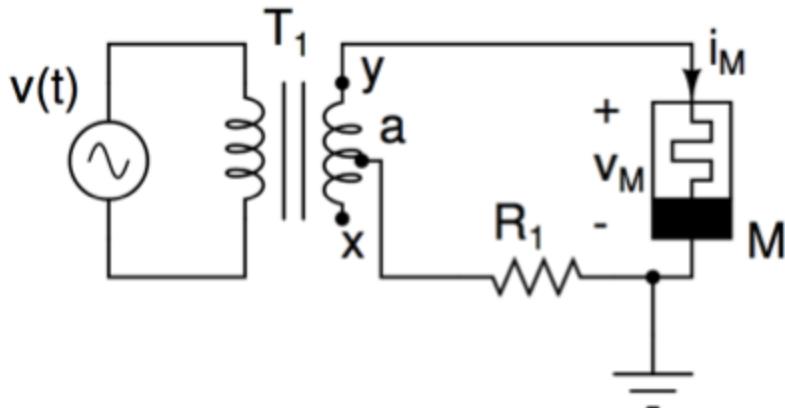


Figure 3. Simulation versus experimental result for memristor pinched-hysteresis (Lissajous) figure.  $v_M, i_M$  are indicated on the plot. Parameters used for simulation:  $\beta = 0.1, \alpha = 0.1, F = 1, \omega = 0.063$  The discharge tube is a Phillips 15 W F15T8.

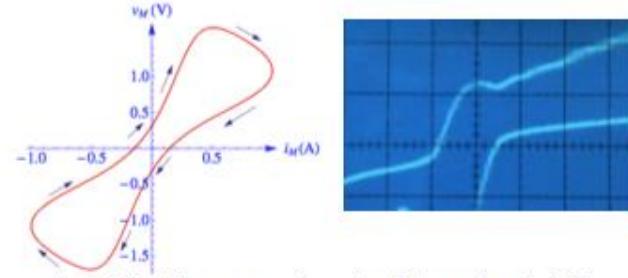


Figure 4. Simulation versus experimental result for memristor pinched-hysteresis (Lissajous) figure. For simulation, we used a 5 H inductor. For the physical setup, we used a 300 H inductor and "zoomed-in" at the origin since the transformer has a measured secondary inductance of 1400 H at 60 Hz.


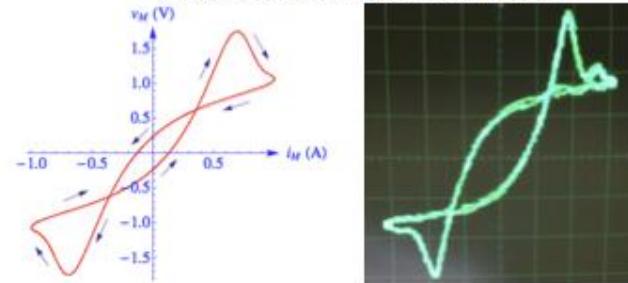


Figure 5. Simulation versus experimental result for memristor pinched-hysteresis (Lissajous) figure. For simulation, we used a 1 F capacitor; for the physical experiment, we show a 100 nF capacitor in parallel.
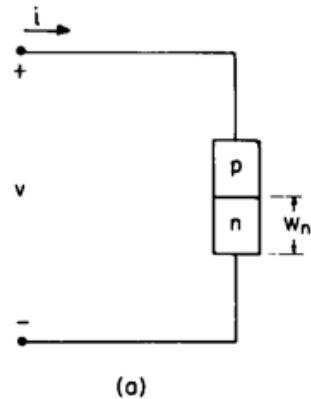
# Non-ideal Memristor : Junction Diode [3]



Simulation of  $R_m(q_m)$  for memristive model of a pn junction diode (Ref.: A Memristive Circuit Model for P-N Junction Diodes, Chua, L. O. and Tseng, Chong-Wei. International Journal of Circuit Theory and Applications, Vol. 2, 367-389 (1974))

Parameters :



$$\begin{aligned}
 N_D &= 10^{15} \text{ cm}^{-3} \text{ (donor concentration)} \\
 \mu_n &= 1350 \text{ cm}^2 / \text{V.sec} \text{ (electron mobility)} \\
 \mu_p &= 480 \text{ cm}^2 / \text{V.sec} \text{ (hole mobility)} \\
 I_S &= 0.5 * 10^{-12} \text{ A} \text{ (diode saturation current)} \\
 \tau_p &= 10^{-7} \text{ sec} \text{ (hole recombination life time)} \\
 V_T &= 26.047 \text{ mV} \text{ (thermal voltage)} \\
 D_p &= \mu_p * V_T \text{ (hole diffusion constant)} \\
 L_p &= \sqrt{D_p * \tau_p} \text{ (hole diffusion length)} \\
 w_n &= 5 * L_p \text{ (width of the n - type region or base width)} \\
 T &= 300 \text{ K} \text{ (Ambient temperature)} \\
 \psi_0 &= 0.9 \text{ V} \text{ (barrier potential)} \\
 n_{i0} &= N_D \text{ (approximately) (equilibrium electron concentration in the n - type region)} \\
 n_i &= 8.367 * 10^8 \text{ cm}^{-3} (@ 300 K) \text{ (intrinsic concentration)}
 \end{aligned}$$

$$p_{n0} = \frac{(n_i)^2 * 300}{n_{i0}} = 2.1 * 10^5 \text{ (equilibrium hole concentration in the p - type region)}$$

$$A = \frac{I_S * l}{q * D_p * p_{n0}}$$

$$\sigma[x_, qm_] := q * \mu_n * n_{i0} + q * \mu_p * \left( p_{n0} + \frac{qm}{A * q * L_p} * \left( \frac{\sinh\left[\frac{w_n}{L_p}\right]}{\cosh\left[\frac{w_n}{L_p}\right] - 1} \right) * \left( \cosh\left[\frac{x}{L_p}\right] - \coth\left[\frac{w_n}{L_p}\right] * \sinh\left[\frac{x}{L_p}\right] \right) \right) \quad (14)$$
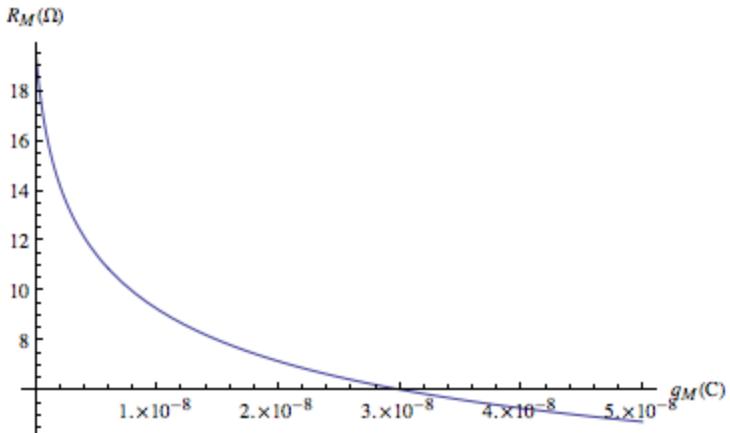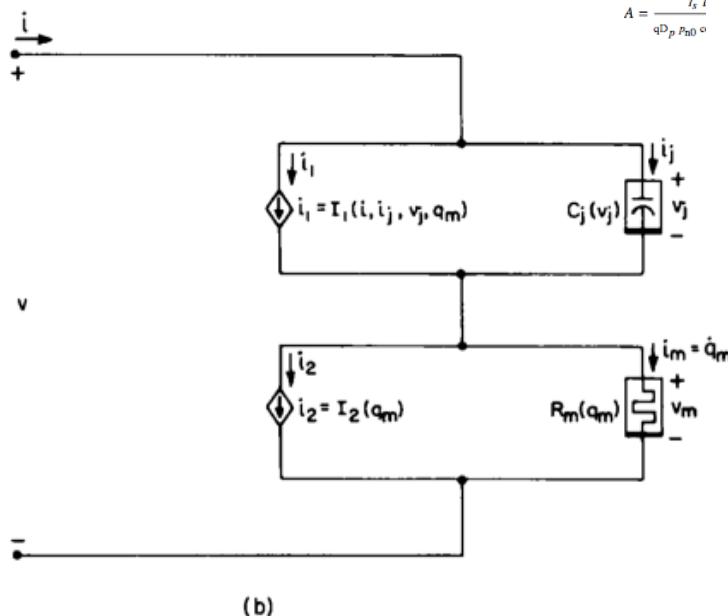
$$R_m[qm_] := \frac{1}{A} * \int_0^{w_n} \frac{1}{\sigma[x, qm]} dx \quad (15)$$



# Ideal Memristor : Josephson Junction [6] [10]


$$E = h \cdot v \quad (16)$$

$$= h \frac{\omega}{2\pi}$$

$$= \hbar \frac{d\phi}{dt}$$

$$2e^- v = \hbar \frac{d\phi}{dt}$$
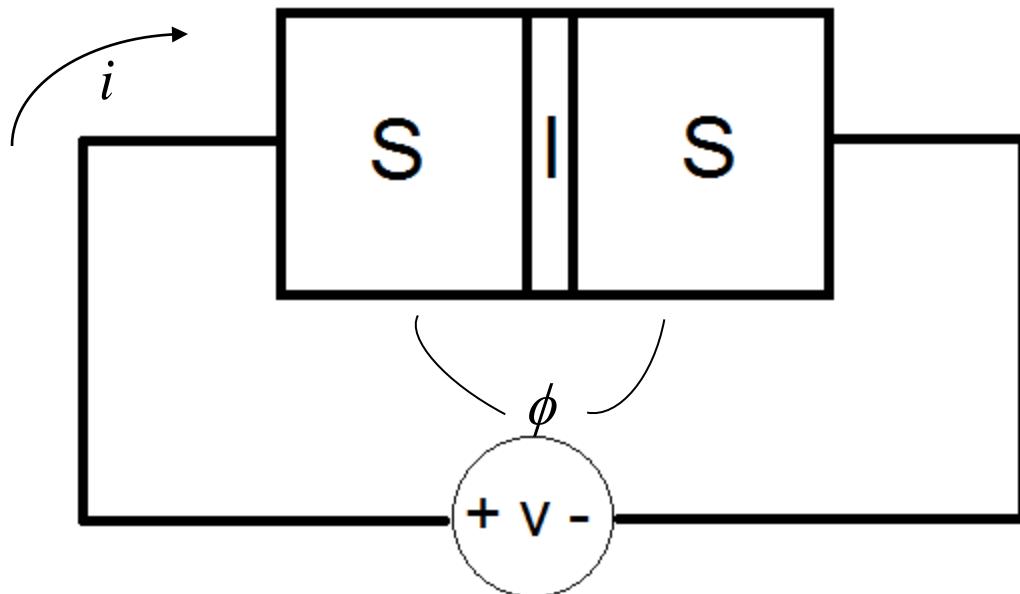
$$\frac{2e^-}{\hbar} v = \frac{d\phi}{dt}$$



$$\frac{d\phi}{dt} = \frac{2e^-}{\hbar} v \quad (17)$$

# Ideal Memristor : Josephson Junction (contd.)

Suppose  $v = 1 \text{ } \mu\text{V}$ .  $f$  (in Hz) for the Josephson junction  $\approx 0.482 \text{ GHz!}$

$$\frac{d\phi}{dt} = \frac{2e^-}{\hbar}(1 \text{ } \mu\text{V})$$

$$\Rightarrow f = \frac{\frac{2e^-}{\hbar}(1 \text{ } \mu\text{V})}{2\pi} \approx 482 \text{ MHz}$$

$$\frac{d\Phi_B}{dt} = v$$

$$\Phi_B \triangleq \frac{\hbar}{2e^-} \phi = k\phi \quad (18)$$




# Ideal Memristor : Josephson Junction (contd.)

In fact, according to the microscopic theory (Josephson 1962), in the case in which  $V$  is constant and the transmission coefficient through the barrier for quasi-particles is small compared to unity,  $j_z$  is given by an expression of the form :

$$j_z = j_1(V) \sin \phi + \{\sigma_0(V) + \sigma_1(V) \cos \phi\} V. \quad . . . \quad (3.10)$$

$$I = I(v) \sin \left( \frac{2e^-}{\hbar} \Phi_B \right) + \left( \sigma_0(v) + \sigma_1(v) \cos \left( \frac{2e^-}{\hbar} \Phi_B \right) \right) v \quad (19)$$
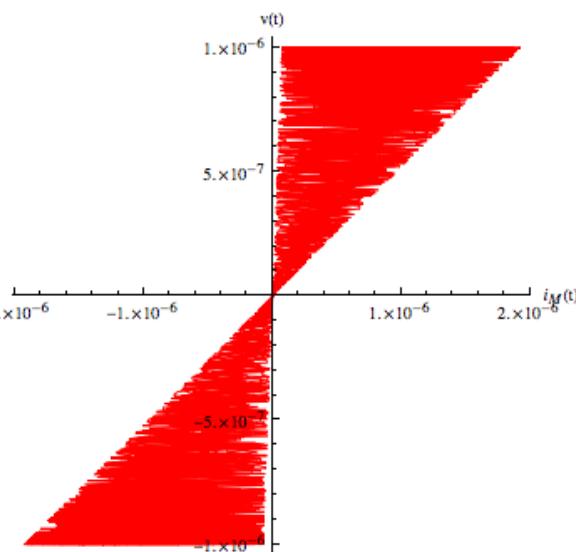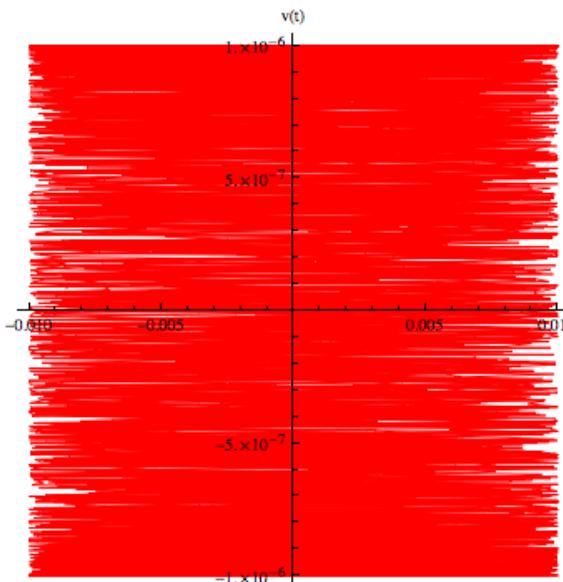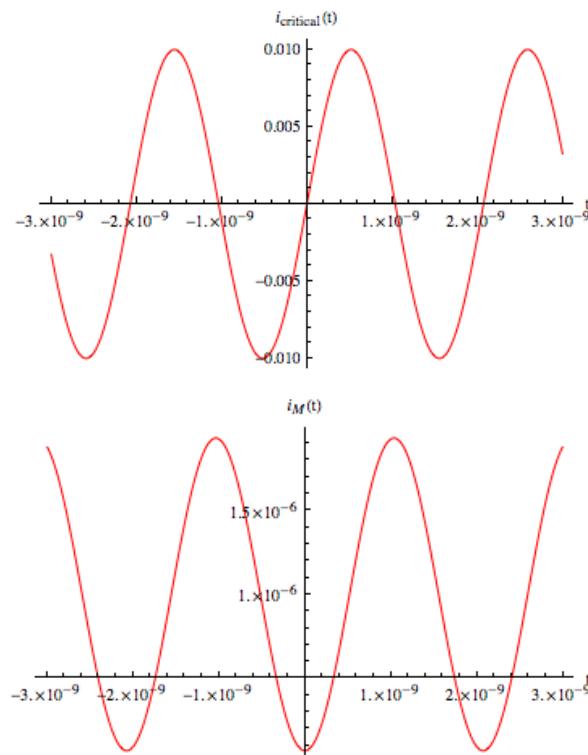
# Ideal Memristor : Josephson Junction (contd.)



On 14 Mar 2014, at 16:28, Bharathwaj Muthuswamy <[muthuswamy@msoe.edu](mailto:muthuswamy@msoe.edu)> wrote:

1. Is it even possible to isolate ONLY the  $\cos(\phi)$  term in the Josephson junction?
2. Does it even make sense to ask if we can isolate the  $\cos(\phi)$  term in the Josephson junction?

Thanks for your email. I think the answer is that the  $\cos(\phi)$  term is non-zero only when there's a non-zero voltage, and then it would be oscillating at a very high frequency ( $2eV/h$ ), which probably makes it unsuitable for your purposes.

Regards, Brian Josephson

-----  
Brian D. Josephson  
Emeritus Professor of Physics, University of Cambridge  
Director, Mind-Matter Unification Project  
Cavendish Laboratory, JJ Thomson Ave, Cambridge CB3 0HE, UK  
WWW: <http://www.tcm.phy.cam.ac.uk/~bdj10>  
Tel. +44(0)1223 337260/337254

# Outline

## I. Background

1. The Fundamental Circuit Elements
2. The Art and Science of Device Modeling

## II. A “Familiar” Example – The junction diode

1. Circuit Model

## III. The Memristor

1. Properties of the Memristor
2. Memristive Devices
3. Memristor Emulator

## IV. Physical Memristors

1. Non-ideal versus Ideal Memristors
2. Non-ideal Memristors:
  - a. Discharge tube
  - b. Junction diode
3. Ideal memristor:
  - a. Josephson junction

## V. Conclusions, Current (future) work and References

# Conclusions

- The memristor is a fundamental circuit element.
- There are physical (electronic) devices that display memristive effects.
- The memristor is a “nonlinear” device (unlike the resistor, capacitor and inductor).

# Current and Future Work

1. Understanding v-i characteristics of discharge tube:  
Circuit for plotting v-i (with Dr. Iu (UWA), Dr. Loo (HKP))
2. Chaos in Muthuswamy-Chua with discharge tube [1] (with Dr. Iu, Dr. Loo and Dr. Corinto (Politecnico di Torino))
3. Identifying ideal memristive behavior in the Josephson junction (with IIT-Chennai and VIT)
4. Complete SPICE model of junction diode with memristor  
(with Dr. Jevtic (MSOE) )
  - Specifically for 3. and 4., use the idea of frequency-power formulae?
5. An electromagnetic field (physical) theory for memristors  
(with Dr. Jevtic and Dr. Thomas (MSOE)).

# References

1. Braun, T. et. al. "Observation of Deterministic Chaos in Electrical Discharges in Gases", *Physical Review Letters*, Vol. 59, No. 6, pp. 613-616, 1987.
2. Chua, L. O. "Memristor-The Missing Circuit Element". *IEEE Transactions on Circuit Theory*, Vol. CT-18, No. 5, pp. 507- 519. September 1971.
3. Chua, L. O. and Tseng, C. "A Memristive Circuit Model for P-N Junction Diodes". *Circuit Theory and Applications*. Vol. 2, pp. 367-389, 1974.
4. Chua, L. O. and Kang, S. M. "Memristive Devices and Systems". *Proceedings of the IEEE*, Vol. 64, No. 2, pp. 209- 223. February 1976.
5. Corinto, F. and Ascoli, A. "Memristive Diode Bridge with LCR Filter". *Electronics Letters*, Vol. 48, No. 14, pp.824–825, DOI: <http://dx.doi.org/10.1049/el.2012.1480>.
6. Josephson, B. "Supercurrents through Barriers". *Advances in Physics*, Vol. 14, No. 56, pp. 419 – 451, 1965.
7. Mader, U. and Horn, P. "A Dynamic Model for the Electrical Characteristics of Fluorescent Lamps", *IEEE Industrial Applications Society – Annual Meeting*, Vol. 2, pp. 1928 – 1934, 1992.
8. Muthuswamy, B. and Chua, L. O. "Simplest Chaotic Circuit". *International Journal of Bifurcation and Chaos*, vol. 20, No. 5, pp. 1567-1580. May 2010.
9. Muthuswamy, B. et. al. "Memristor Modelling". *Proceedings of the 2014 International Symposium on Circuits and Systems*, Melbourne, Australia, June 1<sup>st</sup> – 5<sup>th</sup> 2014.
10. Penfield, P. "Frequency Power Formulas for Josephson Junctions". MIT Technical Report – *Micrometer and Millimeter Wave Techniques*, QPR 113, 1973.
11. Strukov, D. B., Snider, G. S., Steward, D. R. and Williams, S. R. "The missing memristor found". *Nature*, vol. 453, pp. 81-83, 1<sup>st</sup> May 2008.

**MANY THANKS TO DR. JEVТИЧ AND DR. THOMAS (MSOE)**  
Questions and Discussion...